

# Chap 3 - Digital Voltmeter

### ■ **Digital voltmeter parameters**

- range
- resolution
- accuracy
- input impedance

### ■ **Digital voltmeter types**

- CC – continuous current
- AC – alternative current
- vector type

### ■ Accuracy specification

Three type of accuracy specification for DMM

- ppm of  $U_X$  + ppm of  $U_{CS}$
- % of  $U_X$  + % of  $U_{CS}$
- % of  $U_X$  + Least significant digit

Reminder:

$$\mathcal{E}_r = \frac{e_{abs}}{U_X} \quad \mathcal{E}_{RAP} = \frac{e_{abs}}{U_{CS}}$$

Absolute error:

$$e_U = \mathcal{E}_r(\%) \cdot U_X + \mathcal{E}_{RAP}(\%) \cdot U_{CS}$$

$$e_U = \mathcal{E}_r(\text{ppm}) \cdot U_X + \mathcal{E}_{RAP}(\text{ppm}) \cdot U_{CS}$$

$$e_U = \mathcal{E}_r(\%) \cdot U_X + e_{LSD}$$

## EIM Chap 3 – Digital Voltmeter

### ■ Performances specification types

#### DC VOLTAGE

ACCURACY 23°C ± 5°C ±(ppm of rdg. + ppm of range)					INPUT RESISTANCE
RANGE	RESOLUTION	90 DAY	1 YEAR		
100.0000 mV	0.1 µV	40 + 35	50 + 35	> 10 GΩ	
1.000000 V	1.0 µV	25 + 7	30 + 7	> 10 GΩ	
10.00000 V	10 µV	20 + 5	30 + 5	> 10 GΩ	
100.0000 V	100 µV	30 + 6	45 + 6	10 MΩ ±1%	
1000.000 V	1 mV	35 + 6	45 + 6	10 MΩ ±1%	

Keithley

Accuracy is expressed as ±(percentage of reading + digits).

#### 1. DC VOLTAGE OR DCV OF RIPPLE FUNCTION

RANGE	RESOLUTION	ACCURACY	INPUT IMPEDANCE
500mV	10 µV	0.02%+4	10MΩ
5V	100 µV		11.1 MΩ
50V	1mV		10.1MΩ
500V	10mV		10MΩ
1000V	100mV		10MΩ

GW-Instek

## EIM Chap 3 – Digital Voltmeter

### ■ Relation between digits number (DMM) and bits number (DAC)

- ideal case

DMM display	N – digit number	$\Delta V$ – display resolution
DAC	n – bits number	$\delta V$ – conversion resol.

$$U_{CS} = U_{REF} \Rightarrow \Delta V = \frac{U_{REF}}{10^N} ; \quad \delta V = \frac{U_{REF}}{2^n} ; \quad \text{cond: } \Delta V = \delta V$$

Exp:  $\begin{cases} U_{CS} = 20V \\ \Delta V = 10\mu V \end{cases} \Rightarrow N = \log_{10} \left( \frac{U_{CS}}{\Delta V} \right) = 5.3 \rightarrow 5\frac{1}{2} ; \quad n = \log_2 \left( \frac{U_{CS}}{\delta V} \right) = 17.6 \text{ bits} ;$

- noisily case :  $U_{RMS\_noise} = \frac{U_{noise\_MAX}}{\sqrt{12}}$  , if  $U_{noise\_MAX} > \Delta V \rightarrow \Delta V$  unreliable

It uses  $\Delta V_{ech} = U_{RMS\_noise} \cdot \sqrt{12}$

Exp:  $U_{RMS\_noise} = 70\mu V \rightarrow \Delta V_{ech} = 70\sqrt{12} \mu V = 242.5\mu V = \delta V_{ech}$

$$N = \log_{10} \left( \frac{U_{CS}}{\Delta V_{ech}} \right) = 4.92 \rightarrow 5 ; \quad n = \log_2 \left( \frac{U_{CS}}{\delta V_{ech}} \right) = 16.33 \text{ bits}$$

## EIM Chap 3 – Digital Voltmeter

### Digital voltmeter type


Digits	3 %	4 %	5 %	6 %
ENOD	3.01	3.61	4.21	4.81
Counts	1,024	4,096	16,384	65,536
Bits	10	12	14	16

## EIM Chap 3 – Digital Voltmeter
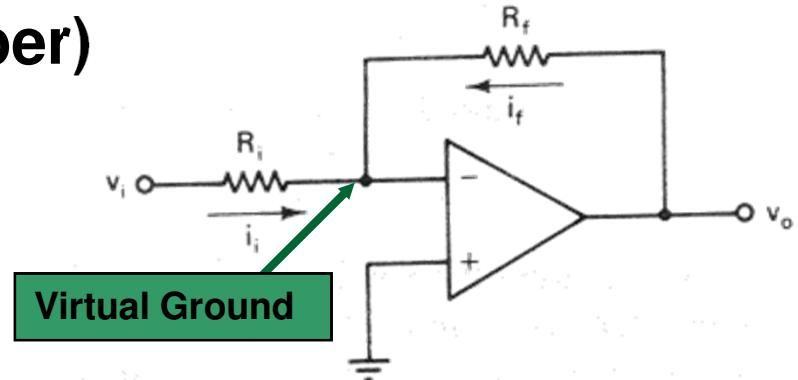
### ■ AO basic circuit (CIA remember)


Inverting amplifier

$$a_U = \frac{V_0}{V_{in}} = -\frac{R_f}{R_i} ; R_{IN} = \frac{V_i}{I_i} = R_i ; R_{out} = 0$$



Non-inverting amplifier

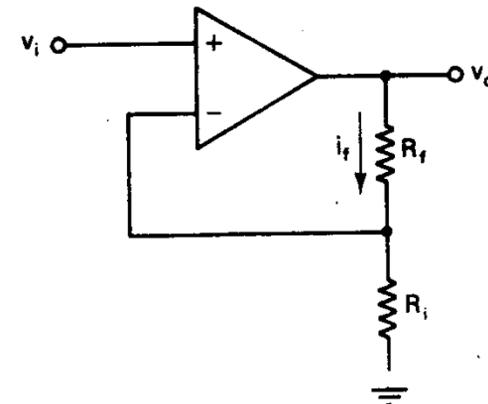
$$a_U = \frac{V_0}{V_{in}} = 1 + \frac{R_f}{R_i} ; R_{IN} \rightarrow \infty ; R_{out} = 0$$



$V_0 = V_{in}$  ;  $R_{IN} \rightarrow \infty$   $\Rightarrow$  buffer function
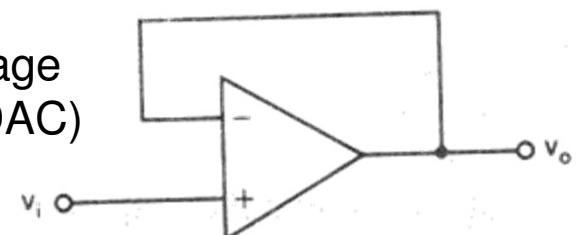
### Applications

- Isolate one circuit from the loading effects of a following stage
- Impedance converter - Data conversion System (ADC or DAC) where constant impedance or high impedance is required



## EIM Chap 3 – Digital Voltmeter


### ■ AO basic circuit (CIA remember)

- open loop output:  $V_X$
- Voltage drop by load:  $V_Y$

$$V_Y = V_X - V_X \frac{R_X}{R_L + R_X} = V_X \frac{R_L}{R_L + R_X}$$


$$R_L \gg R_X \Rightarrow V_Y \approx V_X$$

Ideal:  $R_X$  low,  $R_L$  very large

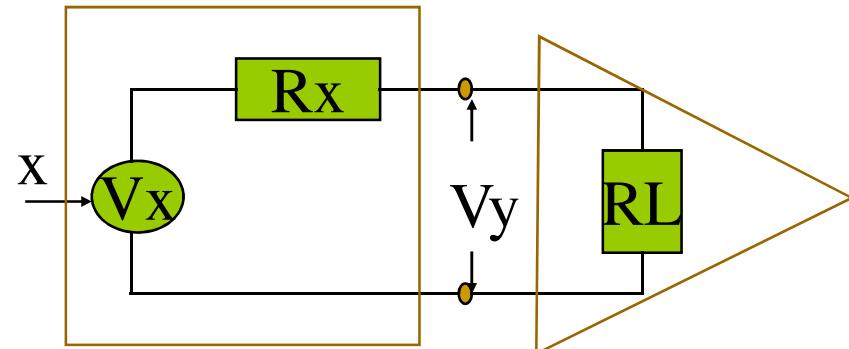
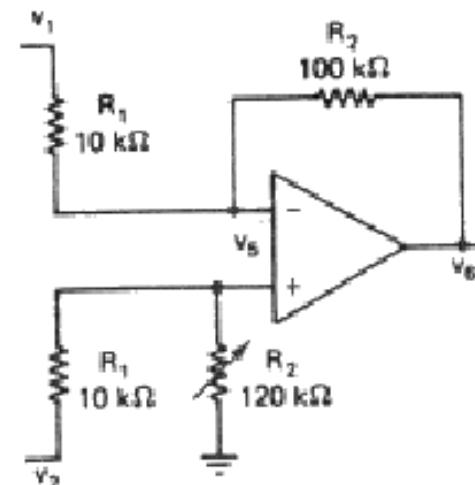
### Differential amplifiers

$$\left. \begin{aligned} V_5 &= V_2 \frac{R_2}{R_1 + R_2} \\ V_5 &= V_1 - R_1 I_1 \\ V_5 &= V_6 + I_1 R_2 \end{aligned} \right\} \Rightarrow V_6 = (V_2 - V_1) \frac{R_2}{R_1}$$




## EIM Chap 3 – Digital Voltmeter

### ■ AO basic circuit (CIA remember)

- CMG = 0 (  $V_1=V_2$     $V_6=0V$  )
- DG =  $R_2/R_1$
- CMRR = DG/CMG (large)
- not high input impedance ()
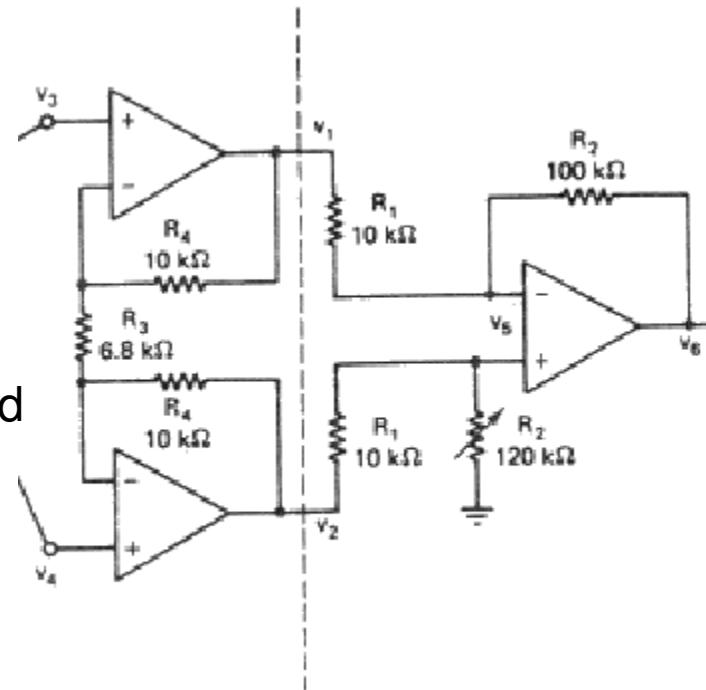
### Instrumentation amplifier


- Two Noninverting Amp + One Differential Amp
- Differential Amp with High Input Impedance and Low Output Impedance




## EIM Chap 3 – Digital Voltmeter

### ■ Rectifiers


Precision half wave rectifier

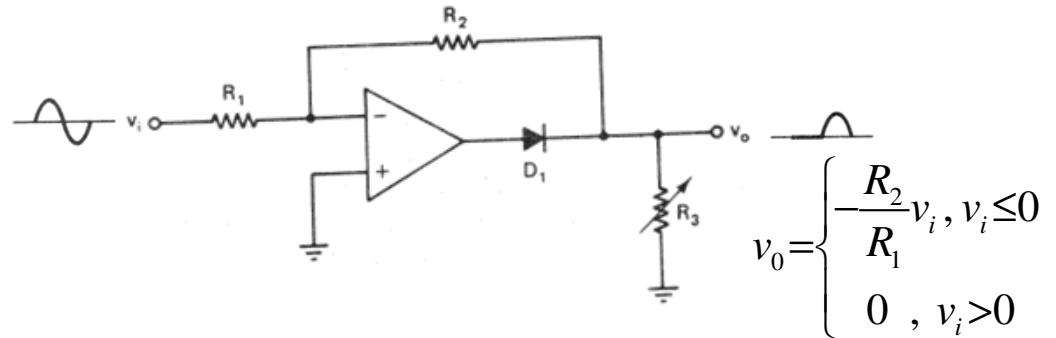

Precision full wave rectifier

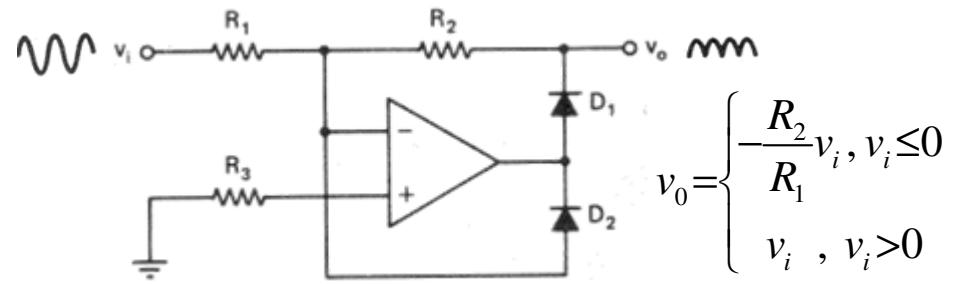


Limiters

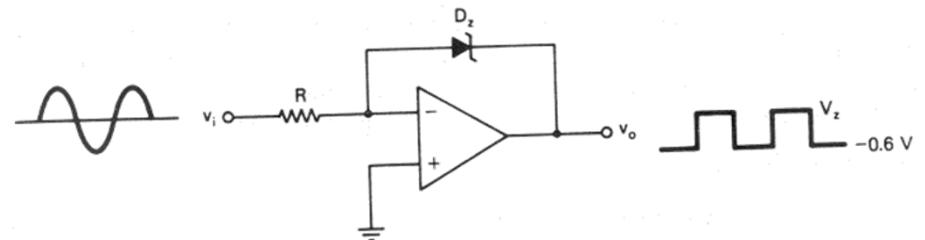

## EIM Chap 3 – Digital Voltmeter


### D.C. digital voltmeter

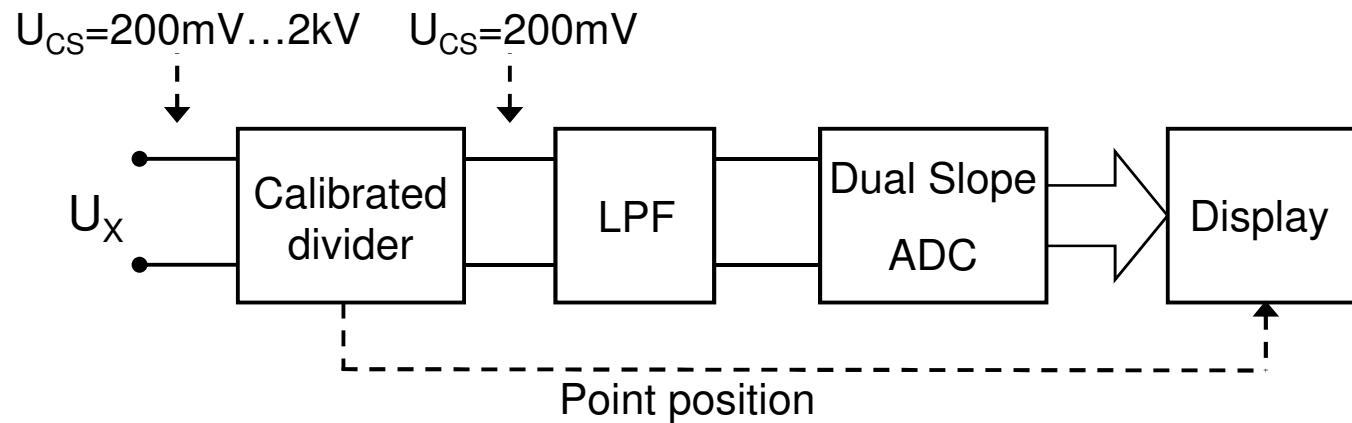

$U_{CS}$  (dual slope ADC)=200mV


## EIM Chap 3 – Digital Voltmeter

### Calibrated voltmeter divider

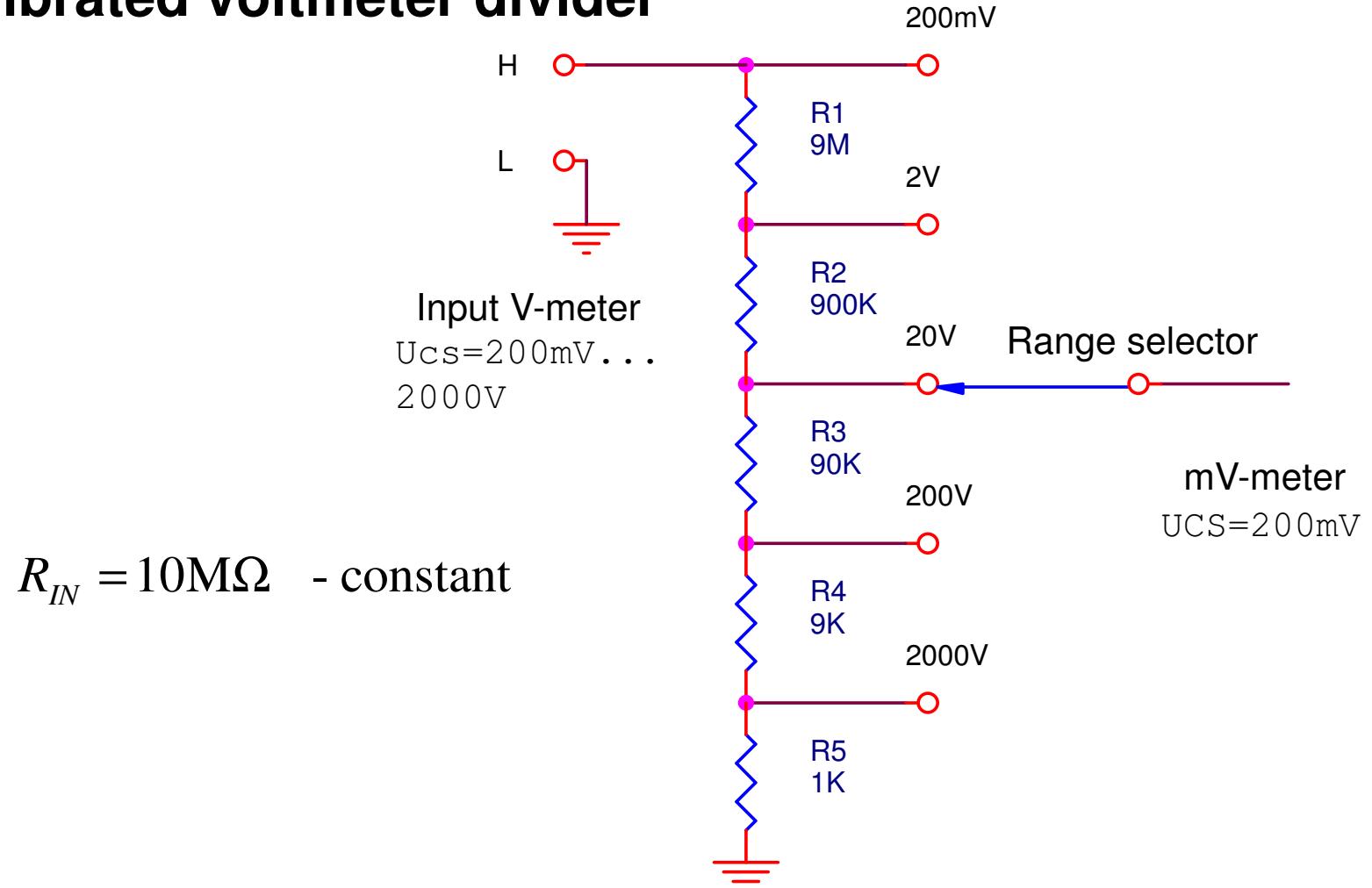

## EIM Chap 3 – Digital Voltmeter

### ■ Auto-range digital d.c. voltmeter

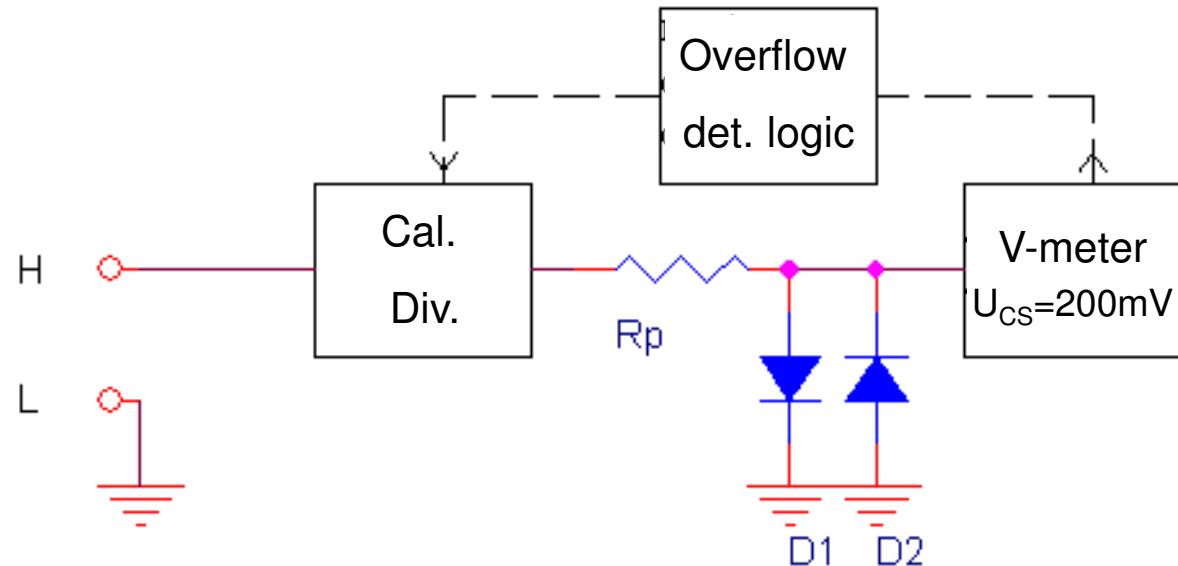

Cal. divider electronic switch

Range:  $U_{CS} = 200\text{mV} - 2\text{V} - 20\text{V}$  etc (range overlapping)

increasing:  $U_{IN} = 0..200\text{mV} \Rightarrow U_{CS} = 200\text{mV}$

$U_{IN} = 200\text{mV}.. 2\text{V} \Rightarrow U_{CS} = 2\text{V}$

decreasing:  $U_{IN} = 2\text{V}.. 180\text{mV} \Rightarrow U_{CS} = 2\text{V}$  (decision hysteresis )

## EIM Chap 3 – Digital Voltmeter


### Dual slope ADC

- Example of schema for positive voltage

$$T_1 = 2^n T_{CK} \quad , \quad t_x = N' T_{CK}$$

$$\frac{1}{RC} \int_0^{T_1} U_x(t) dt = -\frac{1}{RC} \int_{T_1}^{T_1+t_x} V_R dt$$

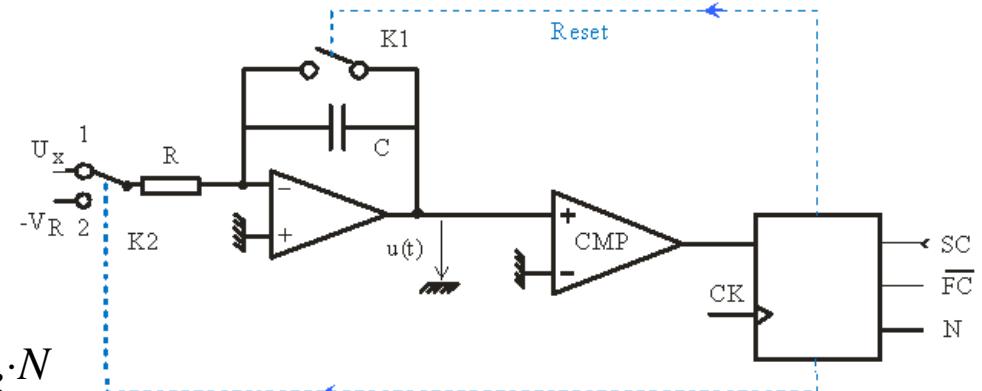
$$\overline{\frac{U_x(t)}{V_R}} = \frac{t_x}{T_1} = \frac{N'}{2^n} \Rightarrow \overline{U_x(t)} = V_R \cdot \sum_{i=1}^n b_i 2^{-i} = V_R \cdot N$$



- Absolute values of R and C don't affect operation
- Conversion time is given by:

$$T_{conv} = (2^n + N') T_{CK} \leq 2^{n+1} T_{CK}$$

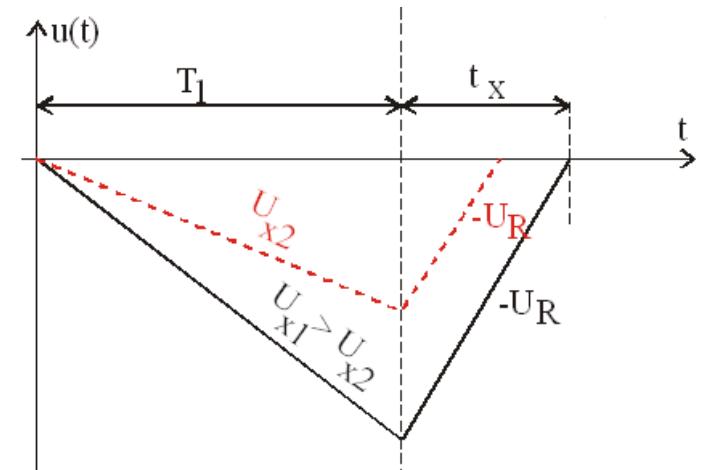
- Digital output word gives average value of  $U_x$  during first integration phase



## EIM Chap 3 – Digital Voltmeter

### Dual slope ADC

- Examples of scheme for bipolar voltage

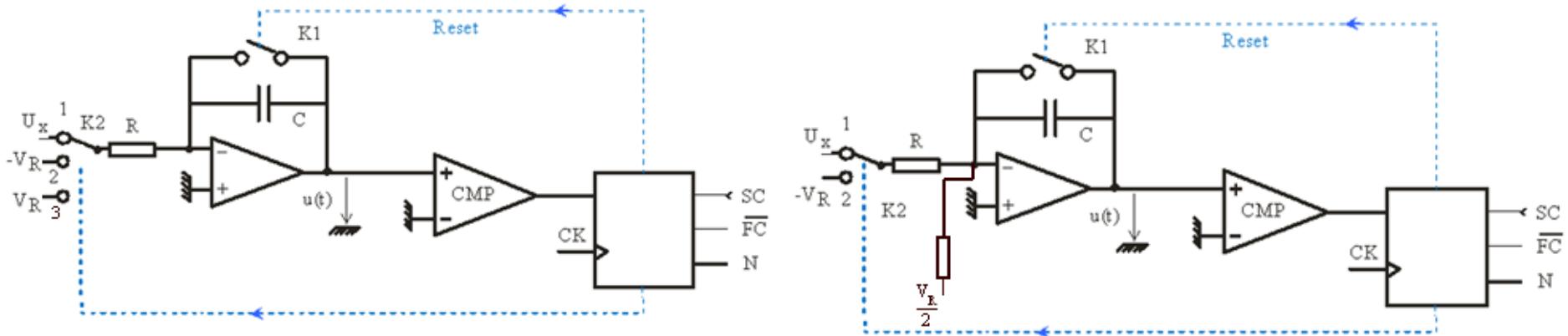


$$T_1 = 2^n T_{CK} \quad , \quad t_x = N \cdot T_{CK}$$

$$-\frac{1}{RC} \int_0^{T_1} U_x(t) + \frac{V_R}{2} dt = -\frac{1}{RC} \int_{T_1}^{T_1+t_x} -V_R + \frac{V_R}{2} dt \Rightarrow \frac{V_R}{2} \cdot \frac{t_x}{RC} = \left( U_x + \frac{V_R}{2} \right) \frac{T_1}{RC}$$

$$U_x = V_R \cdot \frac{t_x - T_1}{2 \cdot T_1} \Rightarrow \begin{cases} U_x = 0 & \text{for } t_x = T_1 \\ U_x = -0,5 \cdot V_R & \text{for } t_x = 0 \\ U_x = 0,5 \cdot V_R & \text{for } t_x = 2T_1 \end{cases}$$

## EIM Chap 3 – Digital Voltmeter

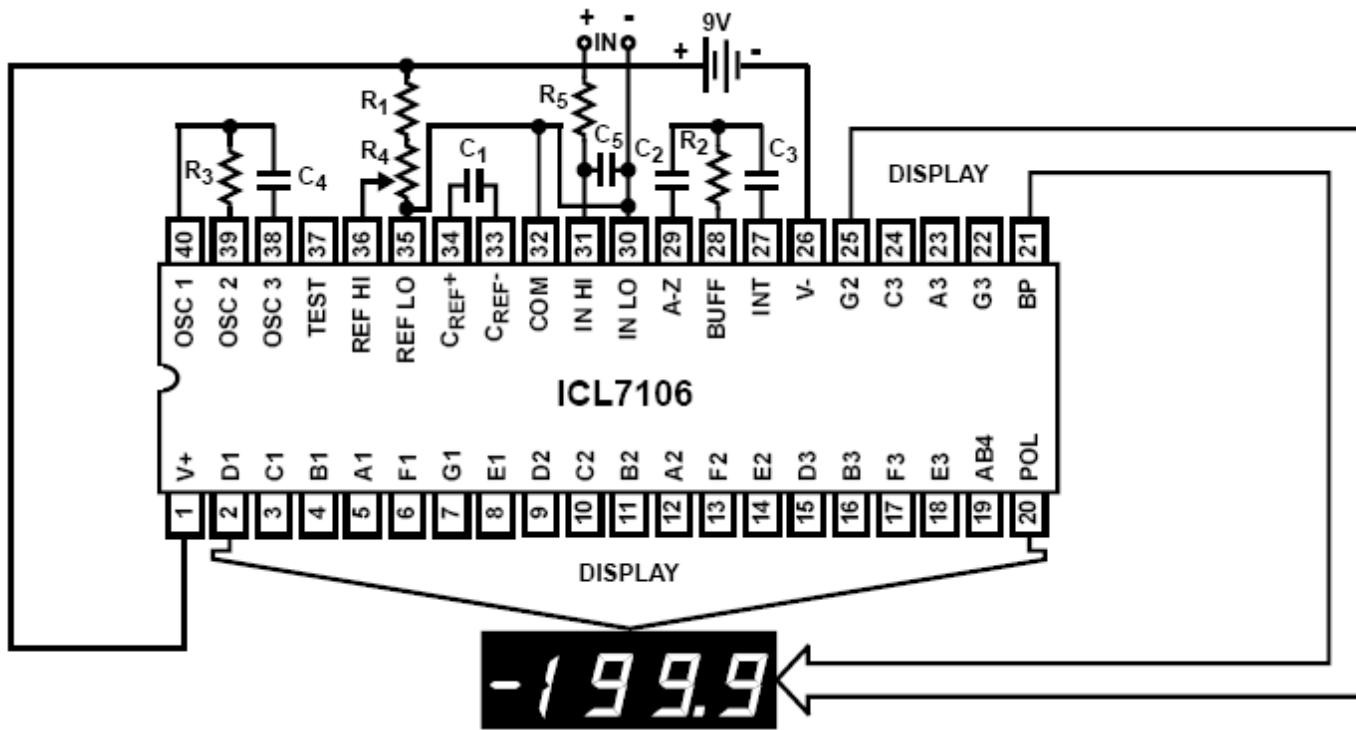
### ■ Example of digital voltmeter with dual slope ADC




$C_1 = 0.1\mu F$   
 $C_2 = 0.47\mu F$   
 $C_3 = 0.22\mu F$   
 $C_4 = 100pF$   
 $C_5 = 0.02\mu F$   
 $R_1 = 24k\Omega$   
 $R_2 = 47k\Omega$   
 $R_3 = 100k\Omega$   
 $R_4 = 1k\Omega$   
 $R_5 = 1M\Omega$

## EIM Chap 3 – Digital Voltmeter

### Functioning principle – ICL7106

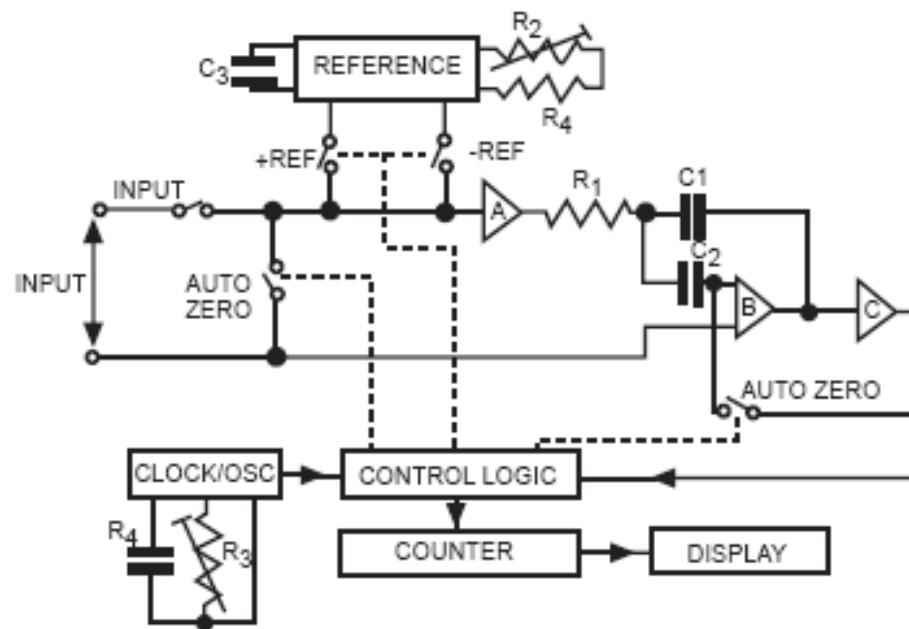


Switches	Phase 0 (AZ)	Phase 1	Phase 2
INPUT	open	close	open
+REF	open	open	funct. of $V_{in}$ sign
-REF	open	open	funct. of $V_{in}$ sign
AUTO-ZERO	close	open	open

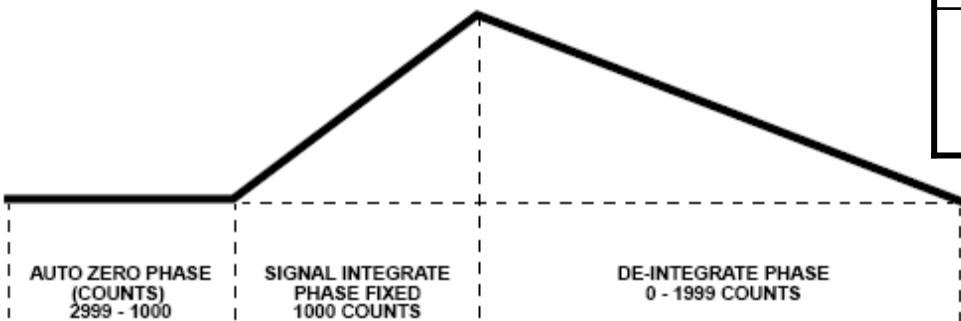

## EIM Chap 3 – Digital Voltmeter
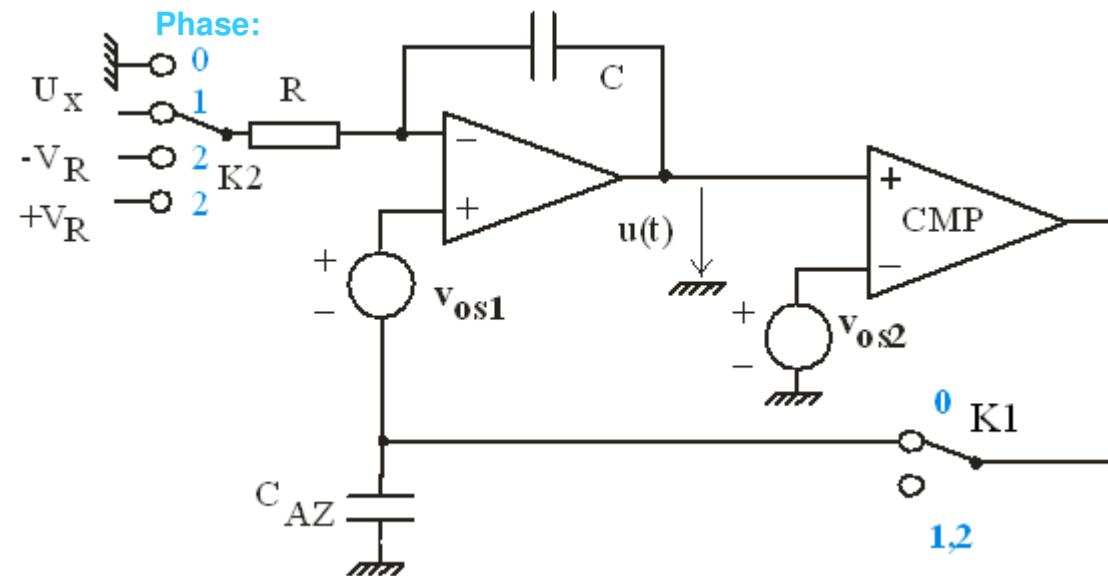
### Techniques for perturbation reduction

- Phase 1 – auto zero ( $K_1=0, K_2=0$ )
- Phase 2 – unknown voltage integrating ( $K_1=1, K_2=1$ )
- Phase 3 - reference voltage integrating ( $K_1=2, K_2=2$ )



### ■ Techniques for perturbation reduction


- selecting integration time in DS - ADC

$$U_x = U_{x0} + u_{ps}(t) = U_{x0} + U_{ps} \cos(\omega t + \phi)$$

$$U_a = -\frac{1}{\tau} \int_0^{T_1} U_x(t) dt = -\frac{1}{\tau} \int_0^{T_1} U_{x0} + u_{ps}(t) dt$$

$$= -U_{x0} \frac{T_1}{\tau} - \frac{U_{ps}}{\tau \omega} [\sin(\omega T_1 + \phi) - \sin(\phi)]$$
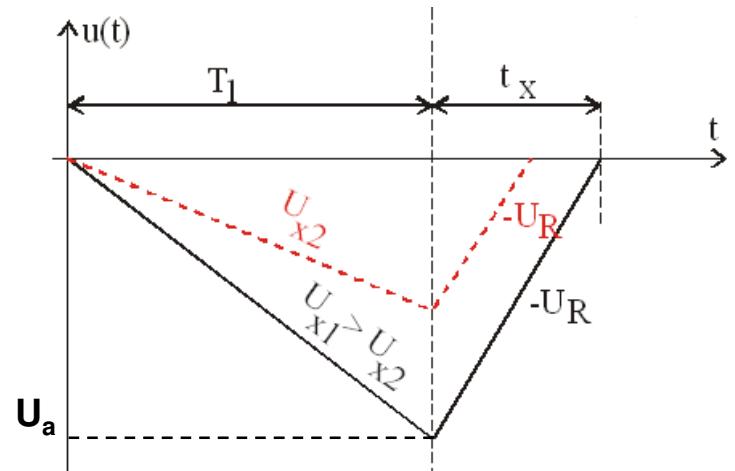
$$= U_{a\_0} + \frac{2U_{ps}}{\tau \omega} \cdot \sin\left(\frac{\omega T_1}{2}\right) \cdot \cos\left(\frac{\omega T_1}{2} + \phi\right)$$



$$\epsilon_{U_x} = \left| \frac{U_x - U_{x0}}{U_{x0}} \right| = \left| \frac{U_a - U_{a\_0}}{U_{a\_0}} \right| = \left| \frac{\frac{2U_{ps}}{\tau \omega} \cdot \sin\left(\frac{\omega T_1}{2}\right) \cdot \cos\left(\frac{\omega T_1}{2} + \phi\right)}{U_{x0} \frac{T_1}{\tau}} \right| = \left| \frac{U_{ps} \cdot \sin\left(\frac{\omega T_1}{2}\right)}{\frac{\omega T_1}{2} U_{x0}} \right| \leq \left| \frac{U_{ps} \cdot \text{sinc}\left(\frac{\omega T_1}{2}\right)}{\frac{\omega T_1}{2} U_{x0}} \right|$$

### ■ Techniques for perturbation reduction

SRR – Serial Rejection Ratio

$$SRR \Big|_{\text{dB}} = -20 \log(\varepsilon_{U_x}) \Big|_{U_{ps}=U_{x0}} = -20 \cdot \log |\text{sinc}(\pi f \cdot T_1)|$$

$$\text{For } f = \frac{k}{T_1} \Rightarrow SRR \Big|_{\text{dB}} \rightarrow \infty$$

Most important perturbation - supply


voltage ( $f_{\text{alim}}=50\text{Hz}$ );

chose  $T_1 = 1/f_{\text{alim}} = 20\text{ms}$

Exp:  $f_{ps} \in [4950\text{Hz}, 5050\text{Hz}]$

$$SRR \Big|_{\text{dB}} \geq -20 \cdot \log \left| \frac{1}{\pi f T_1} \right| \approx 50\text{dB}$$

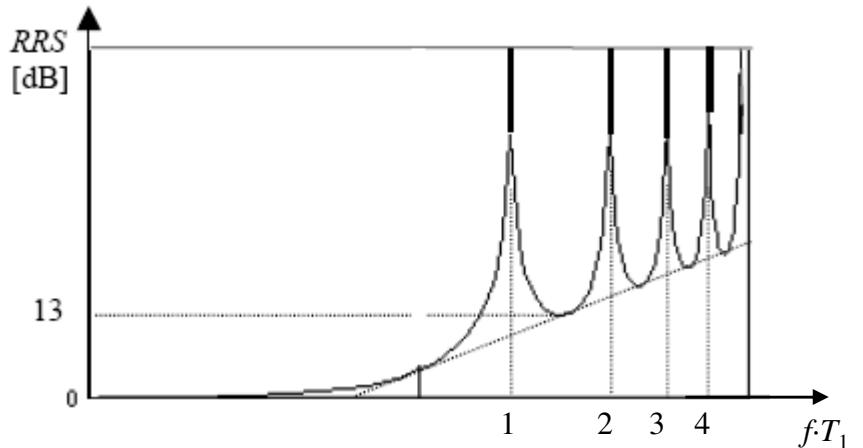
- disadvantage: increase measurement time


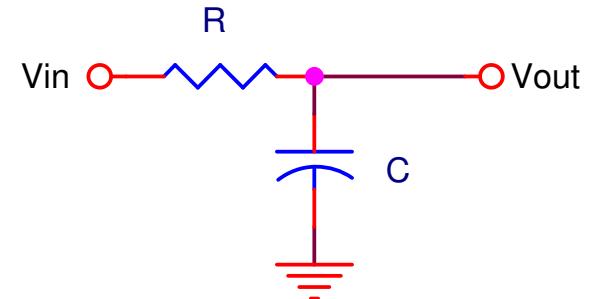
### ■ Techniques for perturbation reduction

- Low pass filter design

$$H(j\omega) = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega\tau}$$



$$RRS_F|_{\text{dB}} \geq 20 \cdot \log \left| \frac{U_{PS}}{U_{PS} \cdot H(j\omega)} \right| = -20 \cdot \log |H(j\omega)|$$

$$\tau = 100\text{ms} \Rightarrow RRS_F = 14\text{dB} \quad (f_{\text{alim}} = 50\text{Hz})$$

$$RRS_{Tot}|_{\text{dB}} = RRS_F|_{\text{dB}} + RRS|_{\text{dB}}$$

$SRR_{tot}$  increases equivalent CMRR

## EIM Chap 3 – Digital Voltmeter

### Exp: Agilent 34401A

Digits	NPLCs	Integration Time 60 Hz (50 Hz)	NMR
4½ Fast	0.02	400.7µs (400 µs)	-
4½ Slow	1	16.7 ms (20 ms)	60 dB
5½ Fast	0.2	3 ms (3 ms)	-
5½ Slow	10	167 ms (200 ms)	60 dB
6½ Fast	10	167 ms (200 ms)	60 dB
6½ Slow	100	1.67 sec (2 sec)	70 dB




RRS (NMRR sau NMR) pentru Agilent 34401A

NPLCs = *Number of Power Line Cycles for 50/60Hz.*

*Obs:* network frequency automating detection


## EIM Chap 3 – Digital Voltmeter

### I-U converter module (DMM)

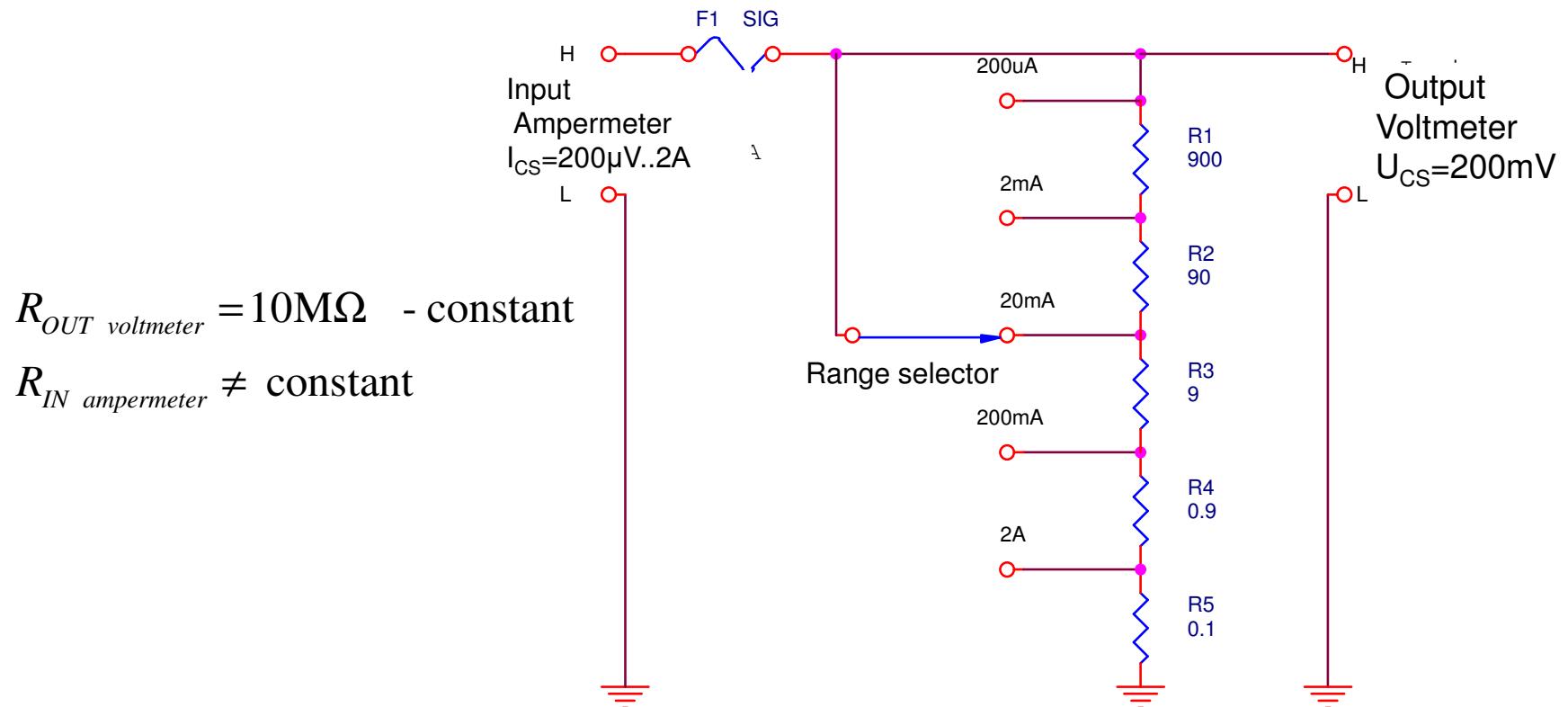

### ■ Small signal d.c. voltmeter (milivoltmeter)


Typical scheme

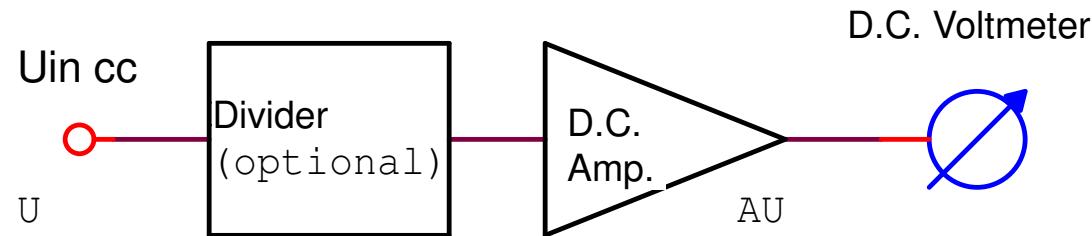

d.c. amplifiers disadvantages:

- self noise
- self offset voltage
- thermal leeway

### ■ D.C. amplifiers with chopper

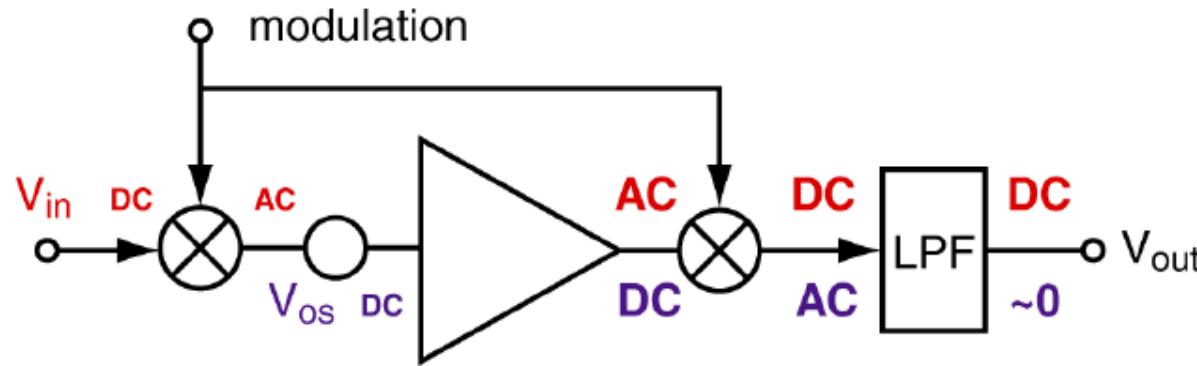


Upper way - util voltage:  $V_{IN}$


Lower way - offset voltage  $V_{os}$  (is rejected):

- Used for d.c. and a.c. low frequency
- Operation: DC → AC conversion (modulation), AC amplifier, AC → DC conversion (demodulation + LPF)

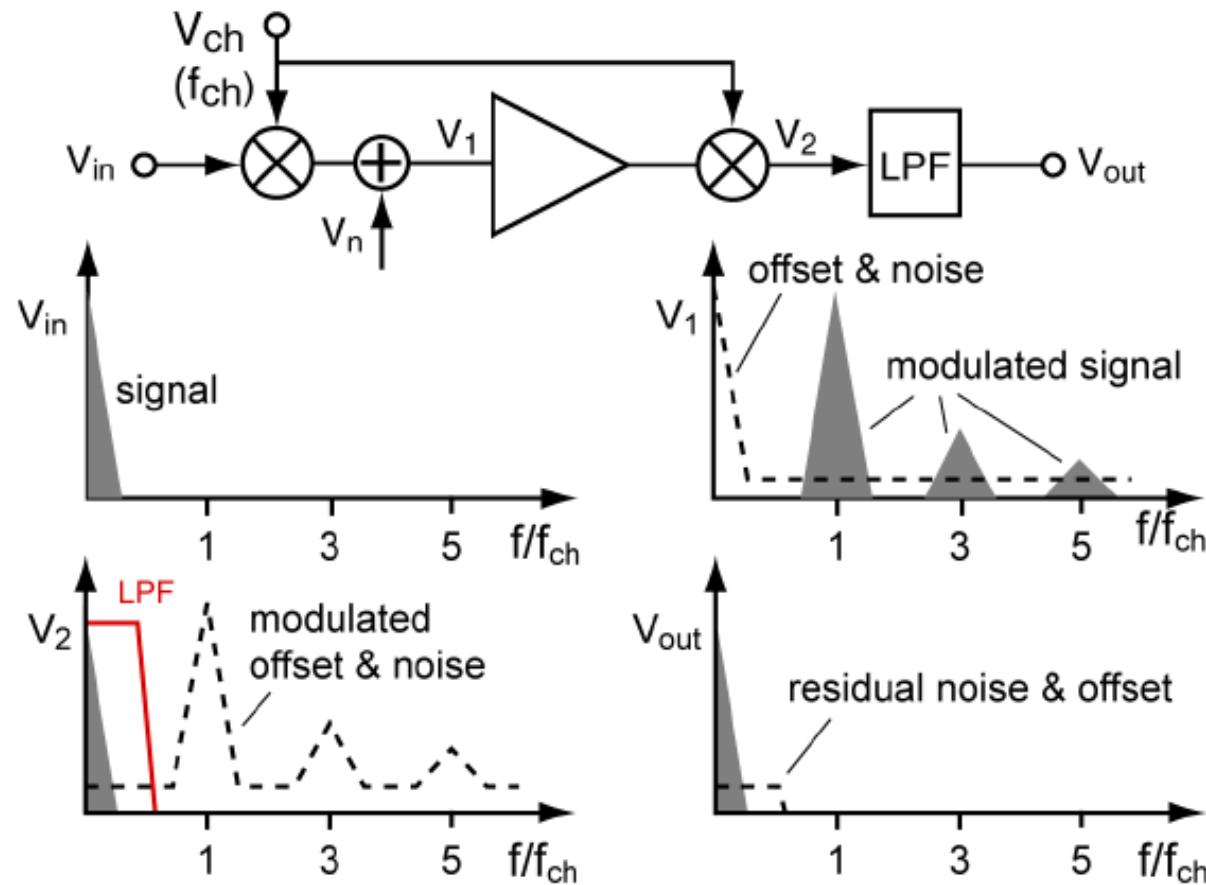■ D.C. amplifiers with chopper - frequency domain




### D.C. amplifiers with chopper

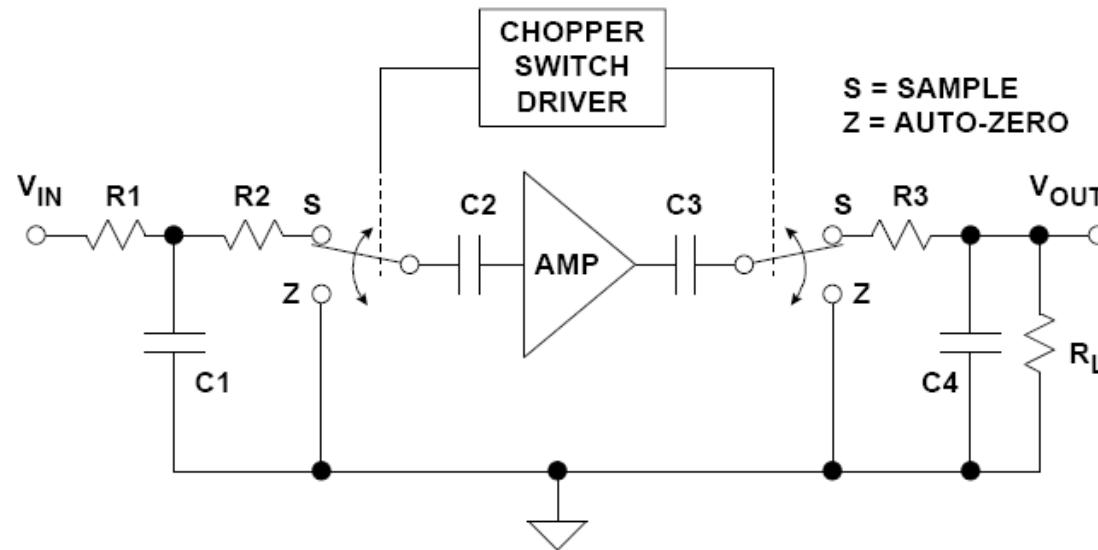

Variant: rectangular modulation/demodulation signal.

- Switch=Z : C2 și C3 charges with offset voltage
- switch=S: C2, C3 voltage compensate offset voltage
- R1, C1 = antialiasing LPF
- R3, C4 = output LPF

### ■ A.C signal (METc remember)

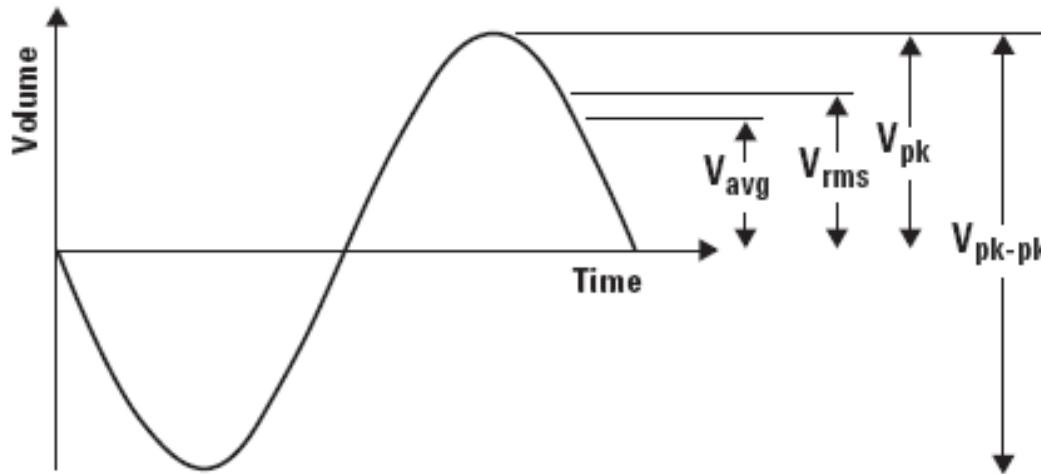

- For  $u(t)=U \sin \omega t$ :

$$V_{\text{med}} = 0 \text{ (unused)}$$

$$V_{\text{ma}} = V_{\text{avg}} = 2U/\pi \text{ (full-wave rect.)}$$

$$V_{\text{ef}} = V_{\text{rms}} = U/\sqrt{2} = 0.707U$$

$$V_V = V_{\text{PK}} = U$$

$$V_{VV} = V_{\text{PP}} = V_{\text{Pk-Pk}} = 2U$$

$$K_F = U_{\text{ef}}/U_{\text{ma}} = \pi / \sqrt{2} = 1.11$$

$$K_V = U_V/U_{\text{ef}} = \sqrt{2}$$

### ■ A.C voltmeter types

Obs: All a.c. voltmeter have gradation for sin wave rms


Types:

- a.m. voltmeter gradated in rms value  $V_{\text{rms}} = V_{\text{ma}} \cdot 1.11$  (introduce important systematic error for non sin wave signals)
- Peak detector voltmeter gradated in rms value  $V_{\text{rms}} = V_{\text{ma}} \cdot 0.707$
- True rms voltmeter – correct indication for all wave forms


### ■ A.C. True rms voltmeter

- thermal effect - thermocouple (slowly, very sensitive of environment factors)
- analog multipliers (ex: Agilent 34405A)
- sampling and digital uP computing (only for repetitive signals)  
(ex: Agilent 34410A, TDS 1001)

Oscilloscope – measurement menu)

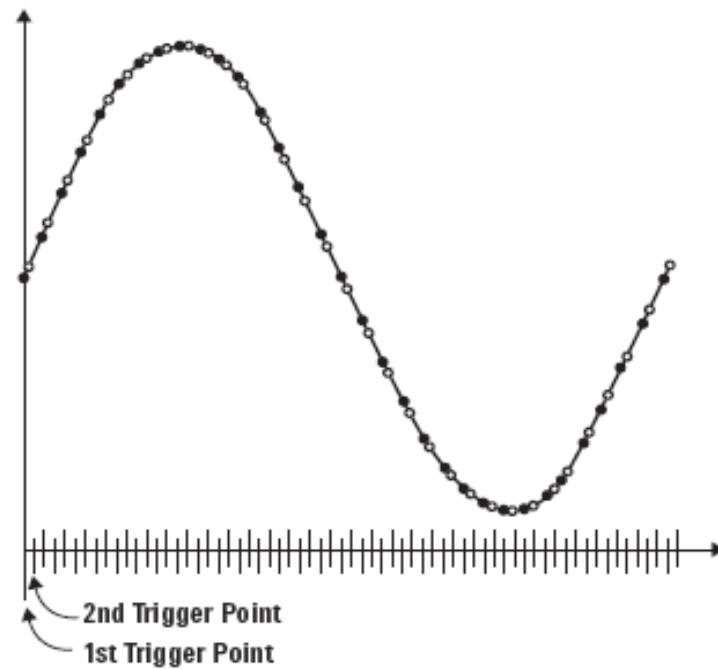

### ■ A.C. voltmeter with D.C. amplifier

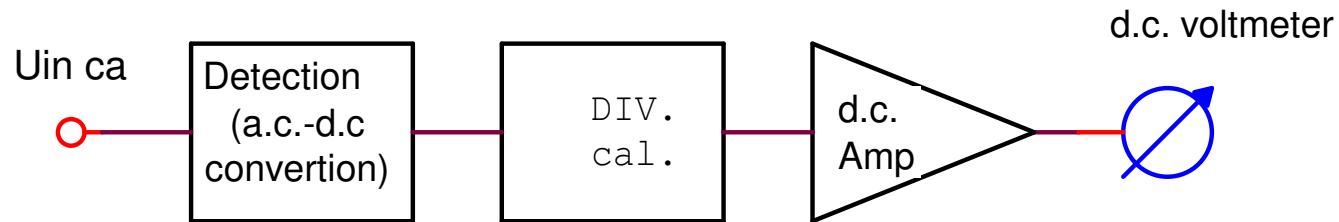


Advantages:

- High bandwidth (GHz)
- Small  $C_{IN}$
- Detector : peak, absolute mean, etc;

Disadvantages:

- Small  $R_{IN}$
- Small sensitivity ( $\times 10$  mV); nonlinear for small signals
- D.C. amplif. gain limited by self noise and thermal leeway

### ■ A.C. voltmeter with a.c. amplifier

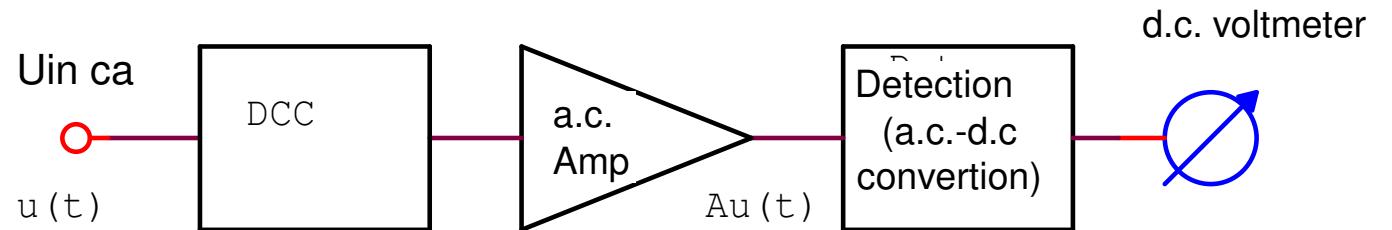

Advantages:

- high sensitivity (due a.c. amplifier), better linearity;
- High  $R_{IN}$ , small  $C_{IN}$
- Detector : peak, absolute mean, etc;

Disadvantages:

- Medium bandwidth (MHz)
- DCC must be compensated

## EIM Chap 3 – Digital Voltmeter


### ■ Cabling – two terminal configuration (Hi, Lo)

$$E_{cm} = V_{Gs} - V_{Gi}$$

After  $E_n$  passivization, measured value

$$U_{nm} = E_{cm}$$
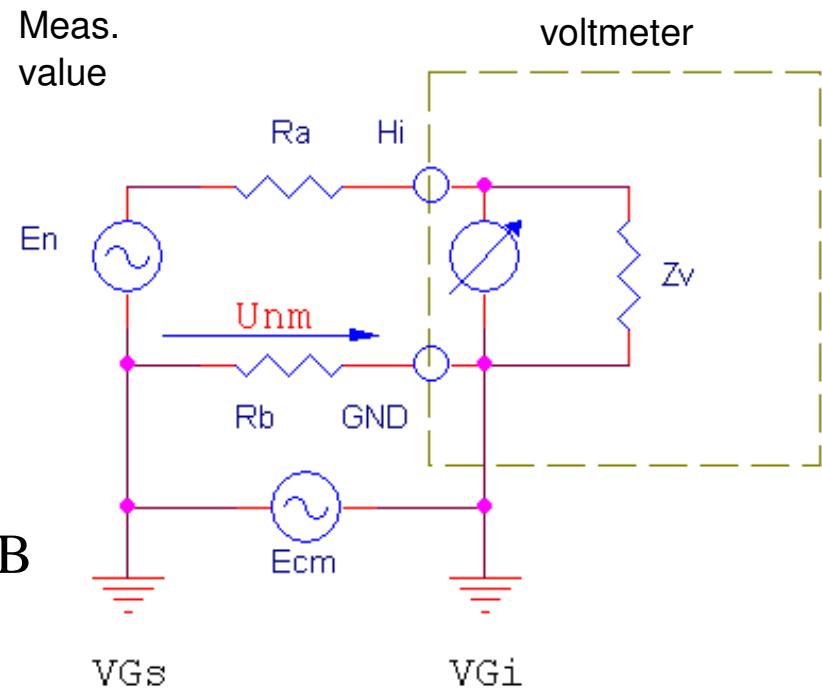
$$CMRR = \frac{E_{cm}}{U_{nm}} = 1 \Rightarrow CMRR_{dB} = 0 \text{ dB}$$



## EIM Chap 3 – Digital Voltmeter

### Cabling – three wire configuration (Hi, Lo, GND)


$$E_{cm} = V_{Gs} - V_{Gi}$$

$$U_{nm} = E_{cm} \frac{R_b}{Z_1 + R_b}$$

$$CMRR = \frac{E_{cm}}{U_{nm}} = \frac{Z_1 + R_b}{R_b} \cong \frac{Z_1}{R_b}$$

$$Z_1 \ll Z_2, \quad I_1 \gg I_2$$

$U_{nm}$  on  $R_a$  is neglected

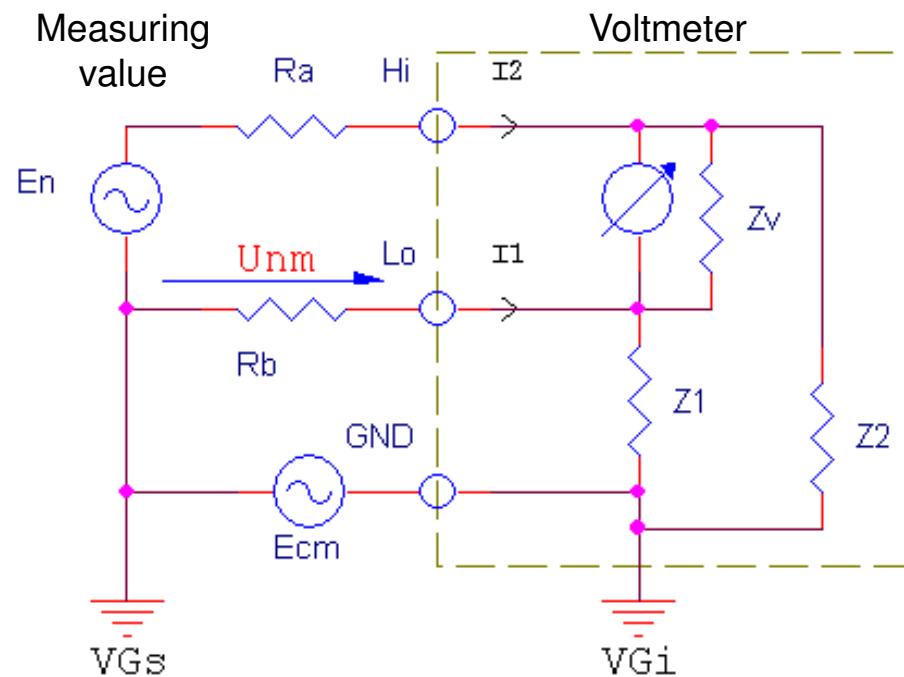

Exp:  $R_b = 1\text{k}\Omega$ ;  $Z_1 = R_1 || C_1$  ( $R_1=109\Omega$ ,  $C_1=2.5\text{nF}$ )

typically d.c. CMRR = 120dB    a.c. ( $f=50\text{Hz}$ ) CMRR = 62dB

## EIM Chap 3 – Digital Voltmeter

### Cabling – three wire configuration (Hi, Lo, GND)

$$\frac{V_2}{r_a} \left( \frac{1}{r_b} + \frac{1}{Z_1} + \frac{1}{Z_2} \right) - \frac{V_1}{r_a} \left( \frac{1}{r_b} + \frac{1}{Z_2} \right) = -\frac{E_{cm}}{r_a} - \frac{E_{cm}}{r_b}$$


$$\frac{V_1}{r_a} \left( \frac{1}{r_b} + \frac{1}{Z_V} + \frac{1}{Z_2} \right) - \frac{V_2}{r_a} \left( \frac{1}{r_b} + \frac{1}{Z_2} \right) = \frac{E_{cm}}{r_a}$$

$$V_1 = E_{cm} \frac{\frac{1}{r_a} \left( \frac{1}{r_b} + \frac{1}{Z_1} \right) - \frac{1}{r_b} \left( \frac{1}{r_a} + \frac{1}{Z_2} \right)}{\left( \frac{1}{r_a} + \frac{1}{Z_V} + \frac{1}{Z_2} \right) \cdot \left( \frac{1}{r_b} + \frac{1}{Z_1} \right) + \left( \frac{1}{r_a} + \frac{1}{Z_1} \right) \cdot \frac{1}{Z_V}}$$

$$\cong E_{cm} \frac{\frac{1}{r_a Z_1} - \frac{1}{r_b Z_2}}{\frac{1}{r_a r_b} + \frac{1}{r_a Z_V}} \cong E_{cm} \left( \frac{r_b}{Z_1} - \frac{r_a}{Z_2} \right)$$

using  $|Z_1|, |Z_2|, |Z_V| \gg r_a, r_b$
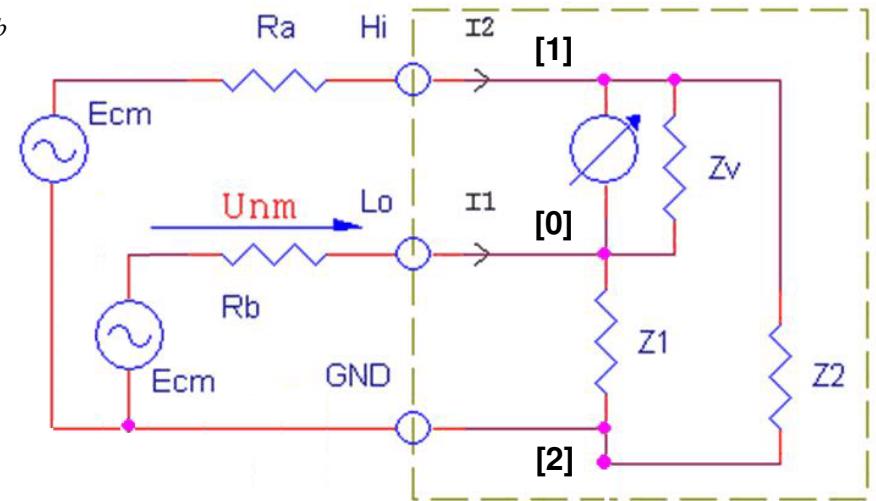
$$U_{nm} = E_{cm} \frac{Z_1}{Z_1 + R_b}$$



$U_{nm}$  on  $R_a$  is neglected


## EIM Chap 3 – Digital Voltmeter

### Cabling - four wire configuration

$$E_{cm} = V_{Gs} - V_{Gi}$$

$$U_{nm} = E_{cm} \frac{Z_4}{Z_4 + R_b}$$
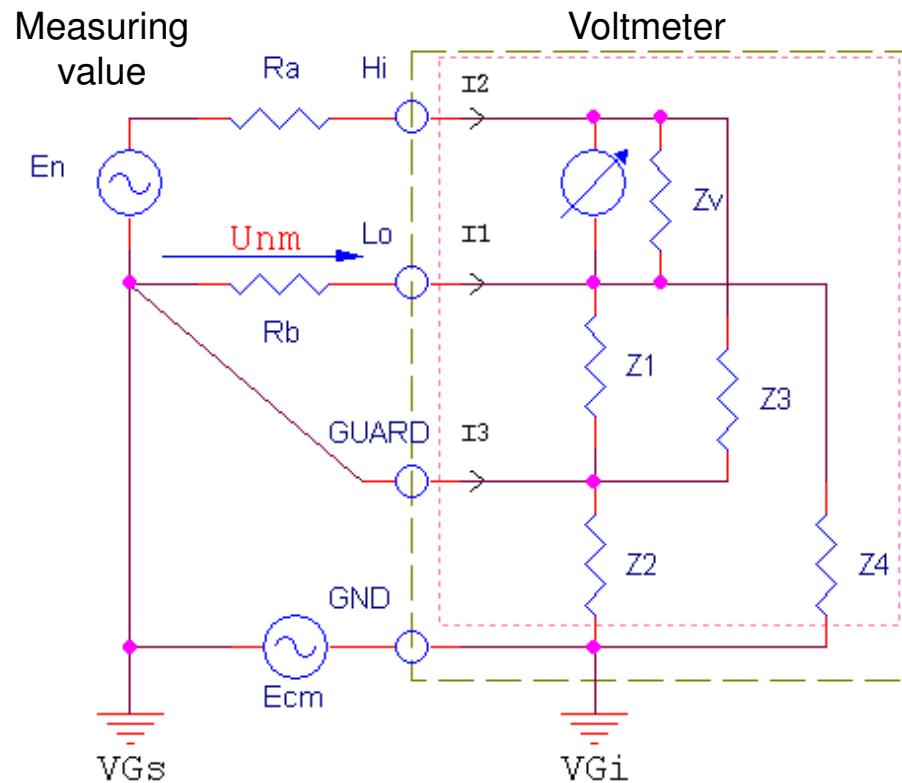
$$CMRR = \frac{E_{cm}}{U_{nm}} = \frac{Z_4 + R_b}{R_b} \cong \frac{Z_4}{R_b}$$



Exp:  $R_b = 1\text{k}\Omega$ ;  $Z_1 = R_1 \parallel C_1$ : ( $R_1 = 109 \Omega$ ,  $C_1 = 2.5 \text{ nF}$ );  $Z_4$  :  $R_4 = 1011 \Omega$ ,  $C_4 = 2.5 \text{ pF}$

typically d.c. CMRR = 120dB    a.c. ( $f=50\text{Hz}$ )    CMRR = 120dB

### ■ Bibliography

- S. Ciochina, *Masurari electrice si electronice*, 1999 ;
- [ham.elcom.pub.ro/iem](http://ham.elcom.pub.ro/iem);
- *Application notes* - National Instruments;