

---

# Digital measurement of Impedance

---

## EMI Chap 4 – Digital measurement of impedances

### ■ Impedance - basics (remember)

- the total opposition of a device or circuit to the flow of an alternating current at given frequency;


$$Z = \frac{\underline{U}}{\underline{I}} = R_S + jX_S = |Z| e^{j\varphi_Z} = \frac{|U|}{|I|} e^{j(\phi_U - \phi_I)}$$

$$|Z| = \sqrt{R_S^2 + X_S^2} \quad ; \quad \varphi_Z = \operatorname{arctg} \frac{X_S}{R_S}$$


$$Y = \frac{\underline{I}}{\underline{U}} = \frac{1}{Z} = G_P + jB_P = |Y| e^{j\varphi_Y}$$

$$G_P = \frac{R_S}{R_S^2 + X_S^2} \quad ; \quad B_P = \frac{-X_S}{R_S^2 + X_S^2}$$


$$Q = \frac{1}{D} = \frac{1}{\operatorname{tg} \delta} = \frac{|P_r|}{P_a} = \frac{|X_S|}{R_S} = \frac{|B_P|}{G_P}$$

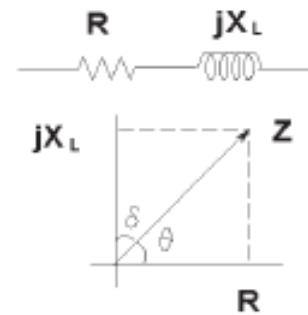


(a) Inductive vector

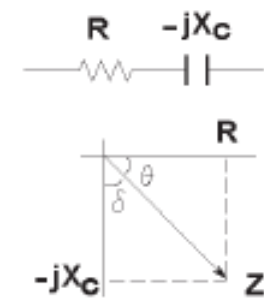

(b) Capacitive vector

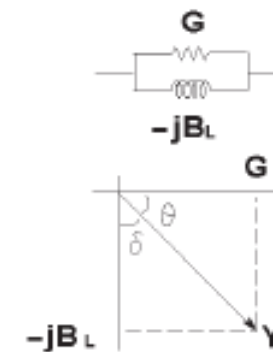




(c) Inductive vector

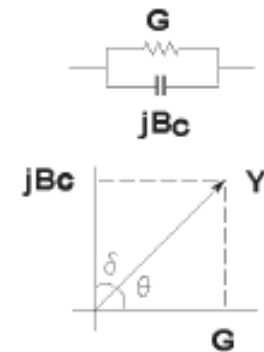

(d) Capacitive vector
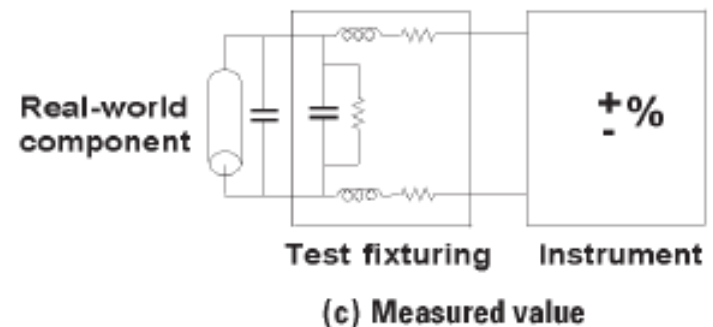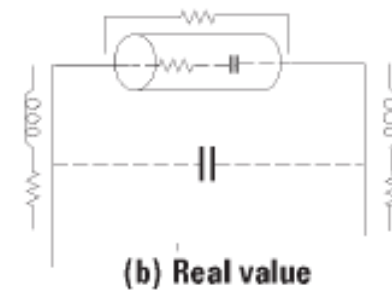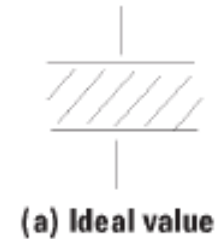
### ■ Impedance value type

- An *ideal* value - the value of a circuit component that excludes the effects of its parasitics; (it has no frequency dependence);
- The *real* value - takes into consideration the effects of a component's parasitics (it is frequency dependent);
- The *measured* value - the value obtained with, and displayed by, the measurement instrument. It contains errors when compared to real value;




## EMI Chap 4 – Digital measurement of impedances

### ■ Component dependency factor (remember)


- frequency of test signal;
- level of test signal;
- temperature, etc.
- Frequency dependency of inductor
- SRF – serial resonant frequency

SRF > frequency of interest

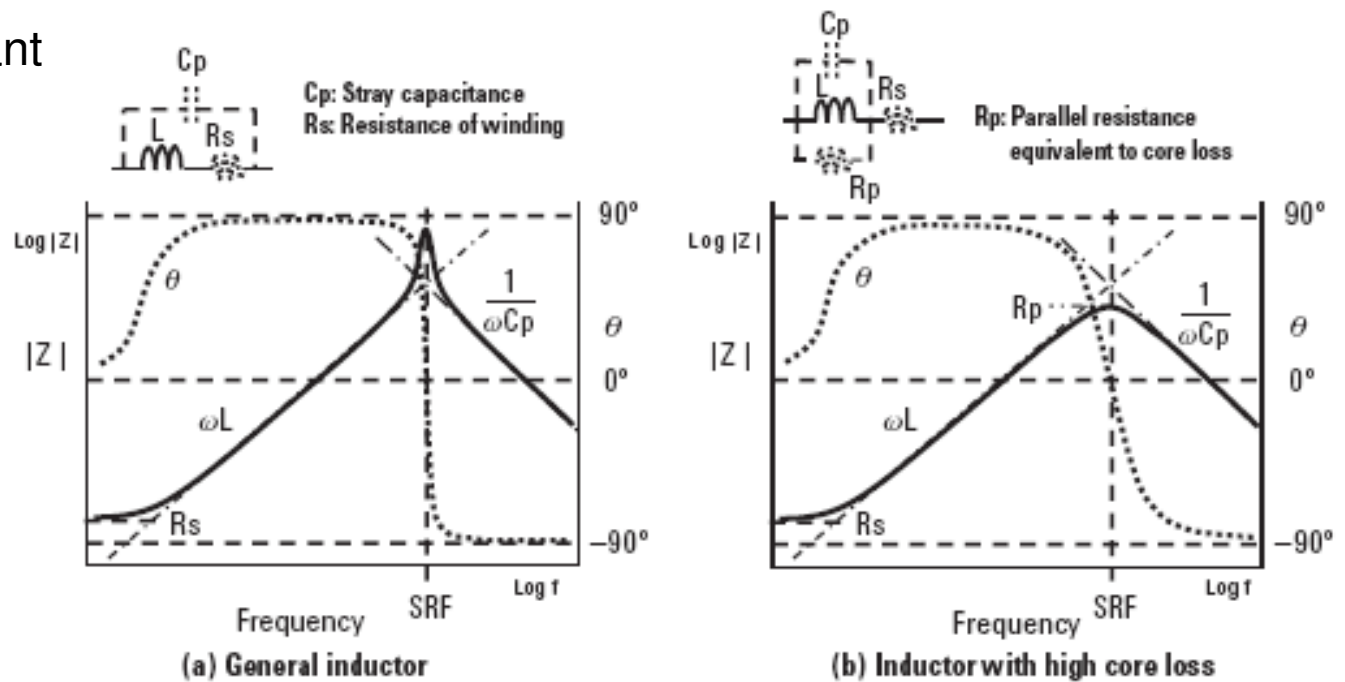
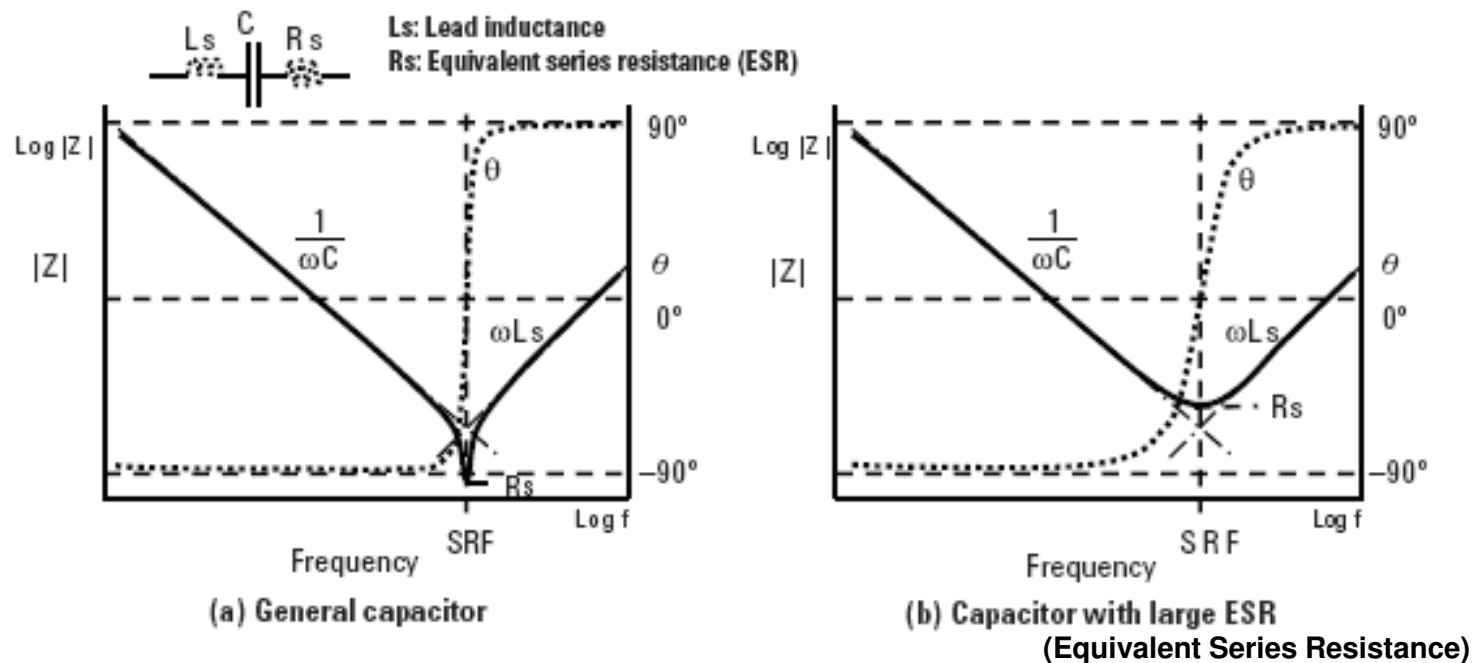
## EMI Chap 4 – Digital measurement of impedances

- **Component dependency factor (cont'd)**
  - Frequency dependency of capacitor




SRF > frequency of interest


## EMI Chap 4 – Digital measurement of impedances

### ■ Component dependency factor (cont'd)

- Frequency dependency

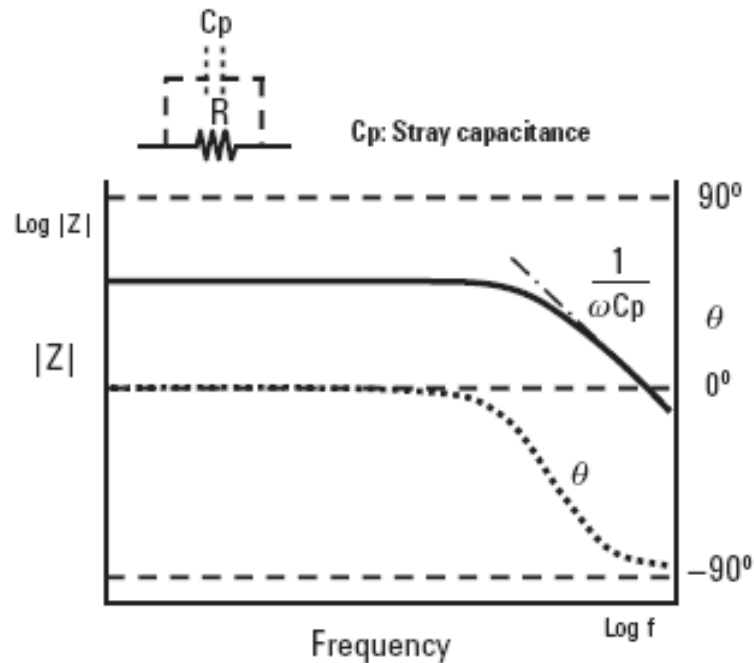

(a) High value resistor

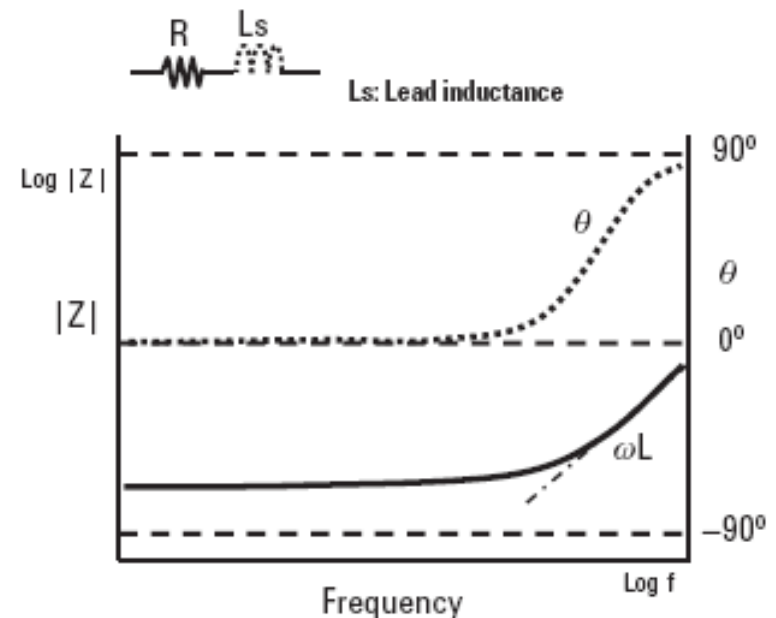


(b) Low value resistor

■ Component dependency factor (cont'd)


- Test signal level

$$C = K\epsilon_0 \frac{S}{d}$$


$$L = \mu_r \mu_0 \frac{N^2 S}{L}$$

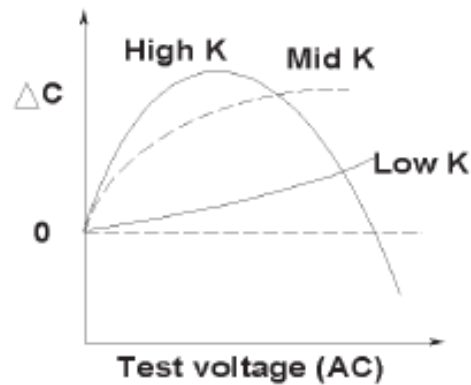

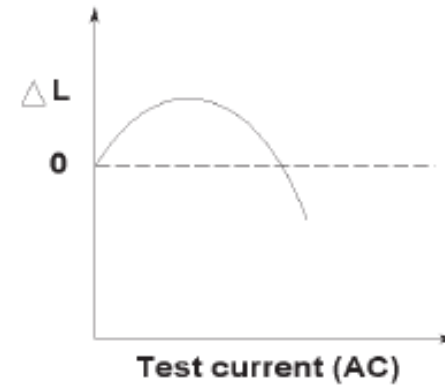
(a) Ceramic capacitor - AC voltage dependency



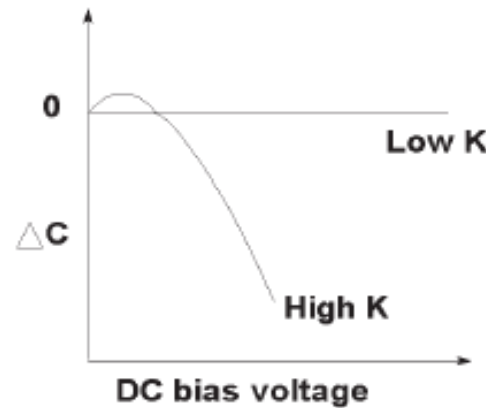(b) Cored-inductor - AC current dependency



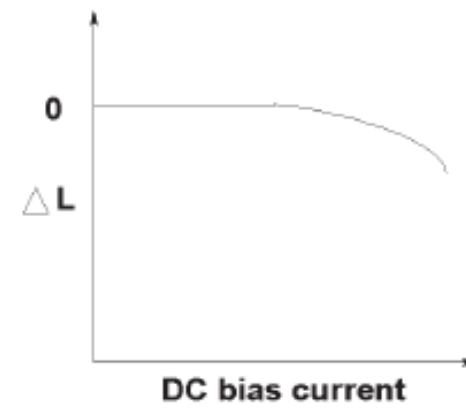(a) Ceramic capacitor - DC bias voltage dependency





(b) Cored-inductor - DC bias current dependency

## EMI Chap 4 – Digital measurement of impedances

### ■ Component dependency factor (cont'd)

- Other dependency factors

Example: capacitor

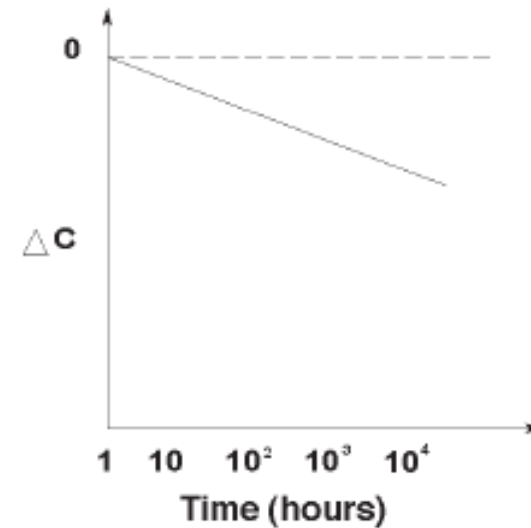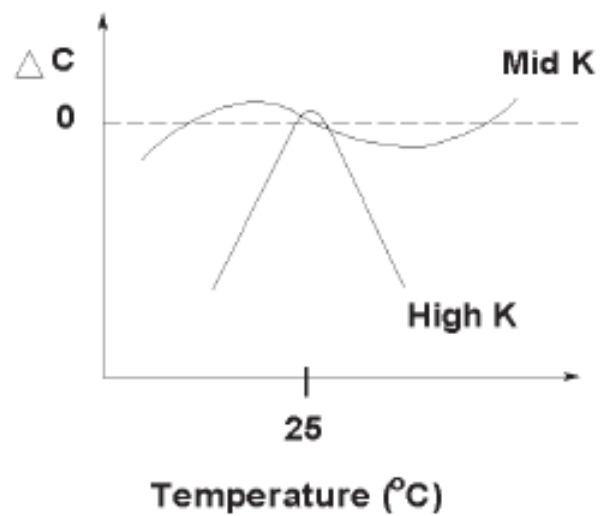



■ Equivalent circuit models (two elements)



$$R_P = R_S (1 + Q^2)$$

$$X_P = X_S \left( 1 + \frac{1}{Q^2} \right)$$

$$\begin{cases} L_P = L_S \left( 1 + \frac{1}{Q^2} \right) \\ C_S = C_P \left( 1 + \frac{1}{Q^2} \right) \end{cases}$$

Measurement parameters:


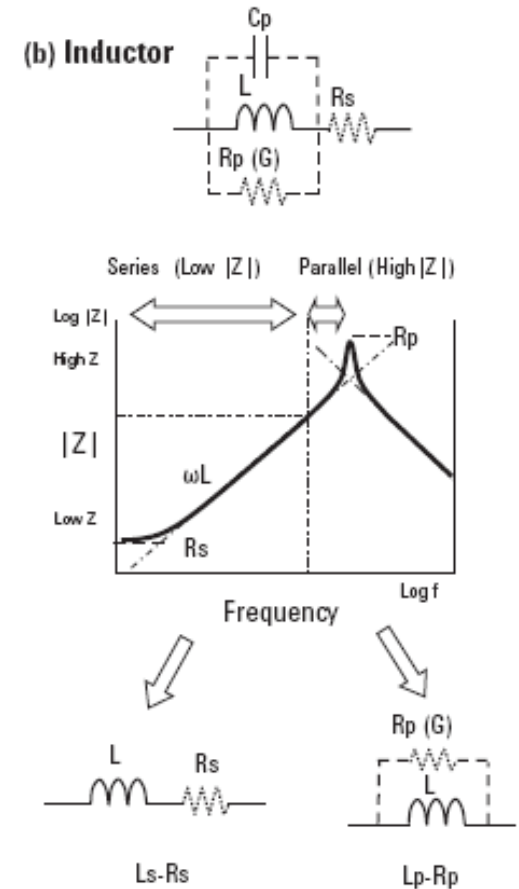
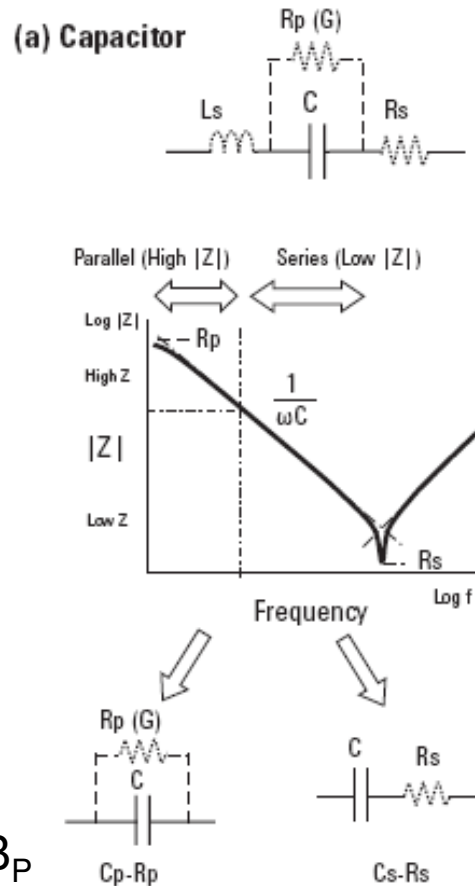
- serial:  $C_S$ ,  $R_S$ ,  $L_S$ ,  $X_S$
- parallel:  $C_P$ ,  $R_P$ ,  $L_P$ ,  $X_P$ ,  $B_P$



■ **Three-element equivalent circuit \***

For high frequency (RF) measuring;

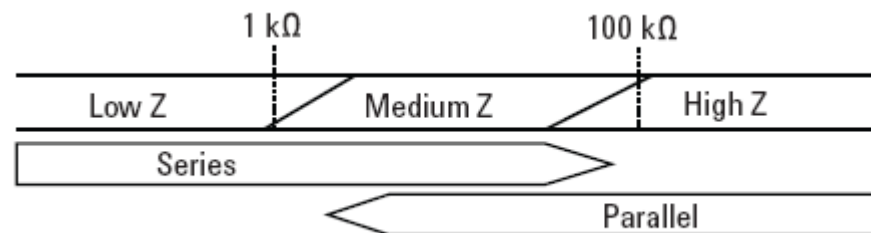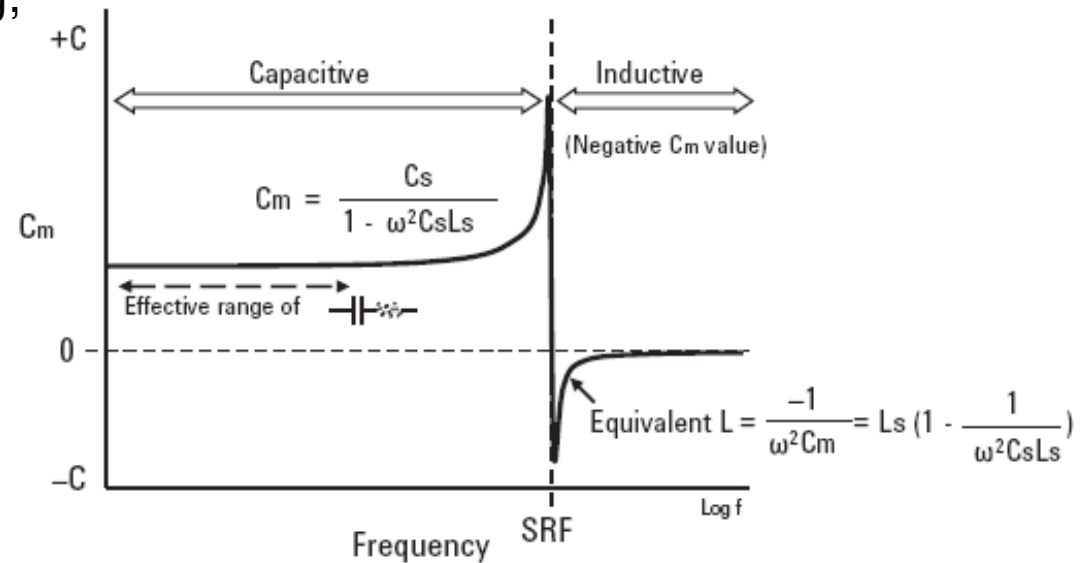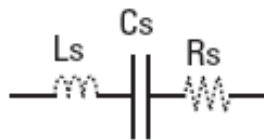- capacitor serial equivalent circuit (Influence of parasitic inductance on capacitor);



- High and low impedance criteria

## EMI Chap 4 – Digital measurement of impedances


### ■ Reactance chart

- shows the impedance and admittance values of pure reactance at arbitrary frequencies.

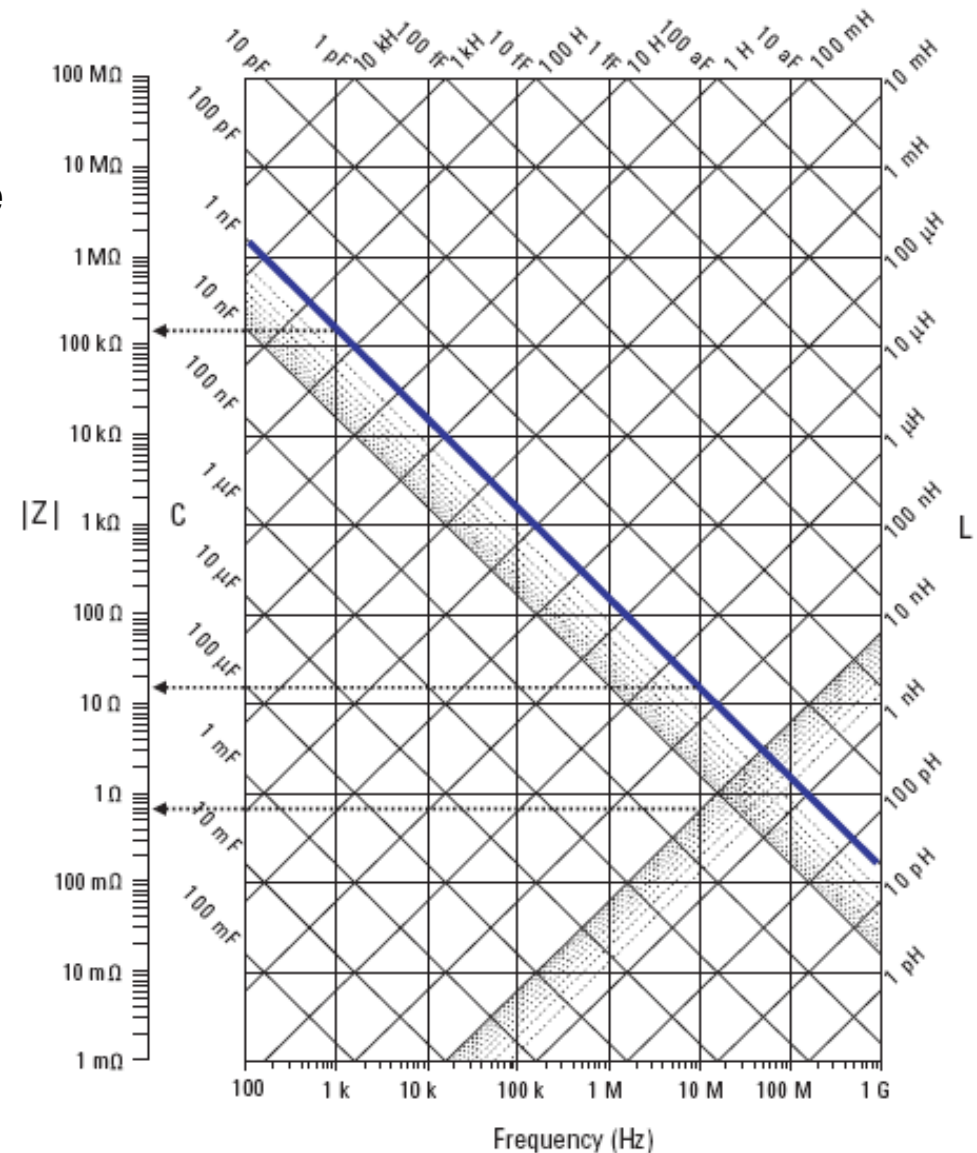*Example:* reactance of a 1nF capacitor is 160k $\Omega$  at 1kHz and 16 $\Omega$  at 10MHz.

- A parasitic series resistance of 0.1 $\Omega$  can be ignored at 1kHz, but it yields a dissipation factor  $D=0.0063$  at 10 MHz.
- a parasitic inductance of 10nH can be ignored at 1 kHz and decreases measured capacitance by 4% at 10MHz .

At the intersection of 1nF line capacitor and the 10nH inductance line is self resonant frequency (SRF).




## EMI Chap 4 – Digital measurement of impedances

### ■ Reactance chart

- useful to estimate measurement accuracy for capacitance and inductance at given frequency.

- impedance measuring instruments measure  $Z=R + jX$  or  $Y=G + jB$  and then compute  $C_s$ ,  $C_p$ ,  $L_s$ ,  $L_p$ ,  $D$ ,  $Q$ ,  $|Z|$ ,  $|Y|$ , etc.

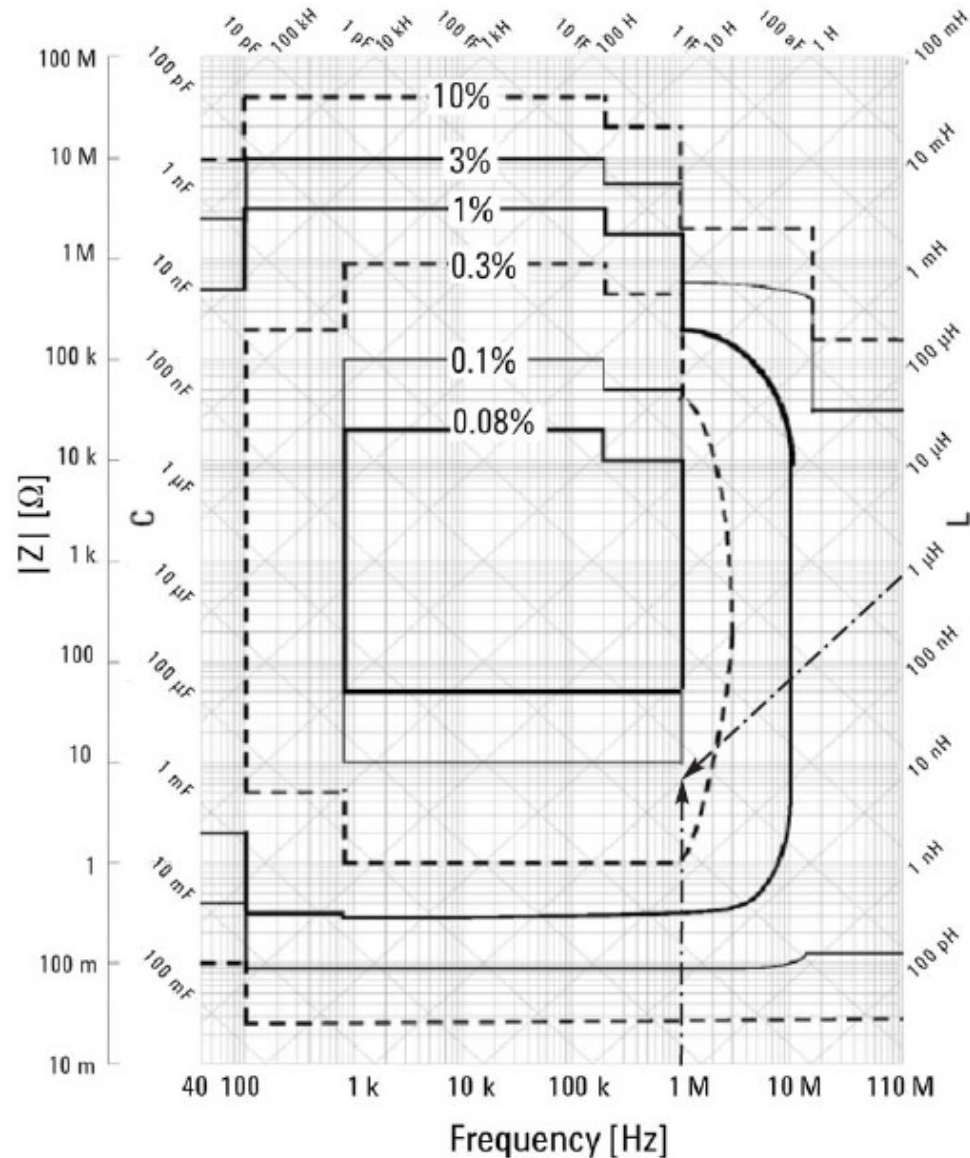- range and accuracy for the capacitance and inductance vary depending on frequency.



■ **Measurement methods (ac)**

- Bridge methods
  - classic bridge
  - Auto-balancing bridge
- I-V methods
  - classic method
  - RF method for low impedance
  - RF method for high impedance
- Network analysis methods
- Resonant methods
  - analog Q - meter
  - digital Q - meter
- methods of conversion  $Z_X \rightarrow T_X$  or  $Z_X \rightarrow f_X$

## ■ Bridge classic method

### Advantages

- High accuracy
- Wide frequency coverage by using different types of bridges [0-300MHz]
- Low cost


### Disadvantages

- Needs to be manually
- Narrow frequency coverage with a single instrument

### Applications

- Standard laboratories

Bridge method

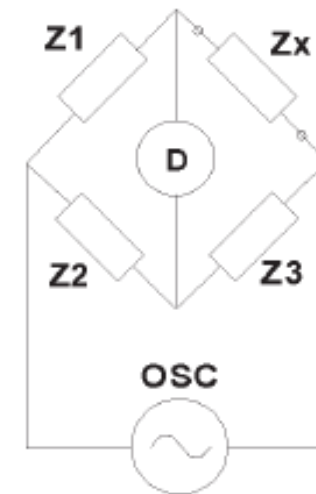

$$I_D = 0 \Rightarrow Z_x = \frac{Z_1 \cdot Z_3}{Z_2}$$

### ■ I-V classic methods

- in practice low loss transformer replace R (to prevent the effects of low value resistor in the circuit);

#### Advantages

- Grounded device measurement
- Suitable to probe-type test needs


#### Disadvantages

- Operating frequency range is limited by transformer 10kHz – 100MHz

#### Applications

- Grounded devices measurement

I-V method

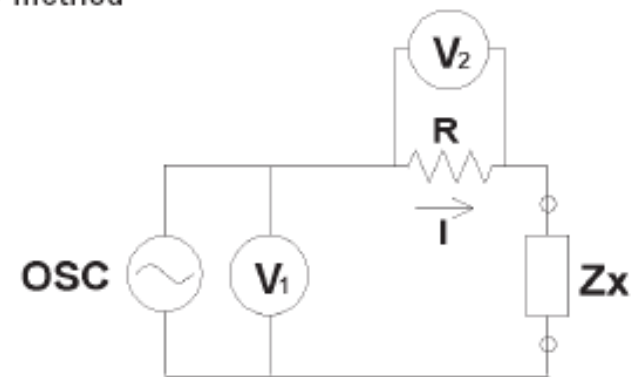

$$Z_x = \frac{V_1}{I} = \frac{V_1}{V_2} R_x$$

## EMI Chap 4 – Digital measurement of impedances

### ■ RF I-V method

- are based on the same principle as the I-V method;
- uses an impedance-matched measurement circuit ( $50 \Omega$ ) and a precision coaxial test port
- R is known

$$Z_x = \frac{V}{I} = \frac{2R}{\frac{V_2}{V_1} - 1}$$

### Advantages



- High accuracy
- Wide impedance range
- High frequencies [1MHz – 3GHz]

### Disadvantages

- Operating frequency range is limited by transformer of probes

### Applications

- RF component measurement

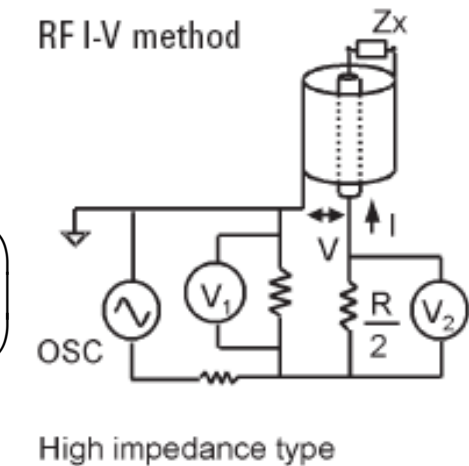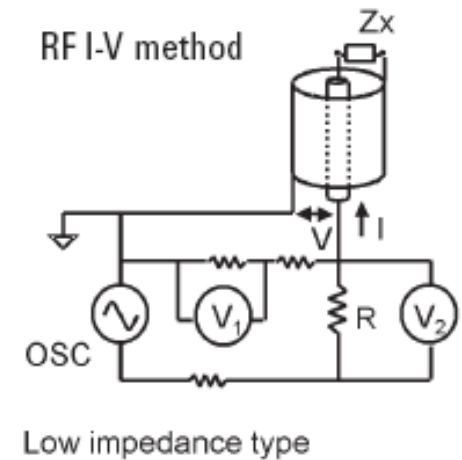



### ■ Network analysis method

- measures reflection coefficient (ratio of an incident signal to the reflected signal);
- uses directional coupler or bridge to detect the reflected signal;
- it is usable in the higher frequency range;

#### Advantages

- High accuracy for  $Z_x$  closed to the characteristic impedance
- High frequency range [300kHz – 500MHz]


#### Disadvantages

- requiring calibration at frequency changing
- Narrow impedance measurement range

#### Applications

- RF component measurement

Network analysis method

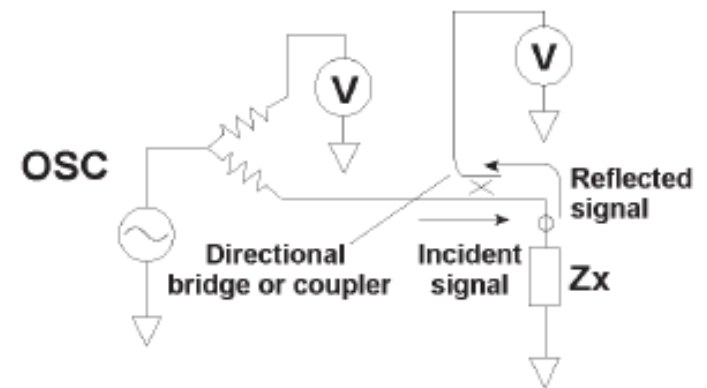

### ■ Resonant method (analog Q-meter)

- the circuit is adjusted to resonance using a tuning capacitor (C)
- Q is measured directly using a voltmeter placed across the tuning capacitor
- $L_x$  can be measured directly
- $C_x$  and extended  $L_x$  can be measured indirectly using serial or parallel connections

$$\begin{cases} C = C_v + C_x \\ L = L_{adj} + L_x \end{cases}$$

#### Advantages

- Good Q accuracy
- High frequency range [70kHz – 50MHz]


#### Disadvantages

- requiring tuning to resonance
- Low impedance measurement accuracy

#### Applications

- High Q devices measurement

Resonant method

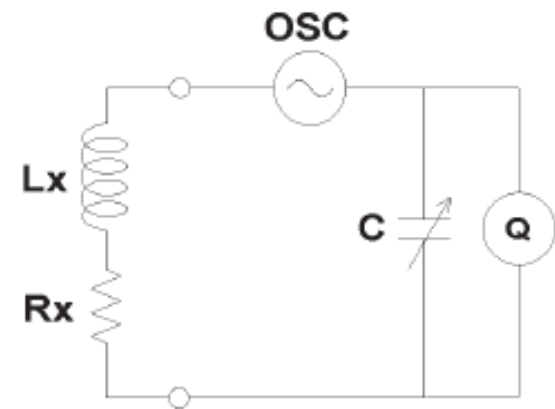

$$L_x = \frac{1}{\omega^2 C}$$

$$Q_x = \frac{U_c}{E} = \frac{1}{R_x \omega^2 C}$$

### ■ Resonant method (digital Q-meter)

- digital Q-meter uses resonance of parallel circuit;
- Theoretical consideration


$$L \frac{d^2 i(t)}{dt^2} + r \frac{di(t)}{dt} + \frac{i}{C} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \xi = \frac{r}{2} \sqrt{\frac{C}{L}} = \frac{r}{2\omega_0 L} = \frac{1}{2Q}$$

$$i(t) = I_0 \exp\left(-\frac{r}{2L}t\right) \cos\left(\omega_0 \sqrt{1-\xi^2} \cdot t + \phi\right)$$

$$\frac{I(t_2)}{I(t_1)} = \frac{I_0 \exp\left(-\frac{r}{2L}t_2\right)}{I_0 \exp\left(-\frac{r}{2L}t_1\right)} = \frac{1}{K} \Rightarrow t_2 - t_1 = \frac{2L}{r} \ln K = \frac{2Q}{\omega_0} \ln K = nT_0 = n \cdot \frac{2\pi}{\omega_0}$$
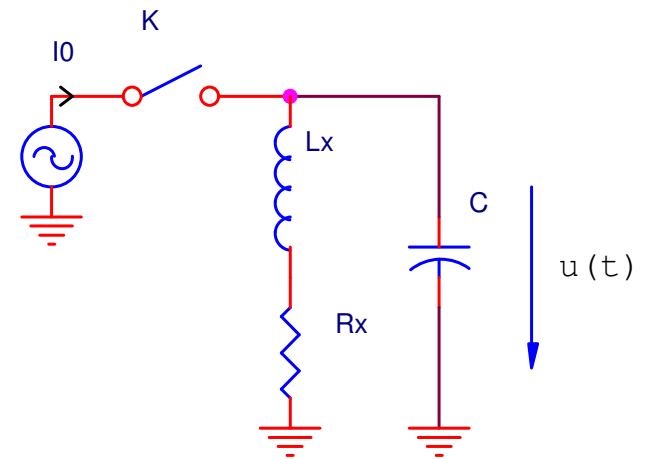
$$\text{if } Q > 3 \Rightarrow \xi < 1/6 \Rightarrow \omega \approx \omega_0 \left(1 - \frac{1}{2}\xi^2\right) \approx \omega_0 \Rightarrow n = \frac{Q}{\pi} \ln K$$






# EMI Chap 4 – Digital measurement of impedances

## Resonant method (digital Q-meter)

- practical consideration

$$u(t) = \frac{I_n}{\omega_n C} \exp\left(-\frac{R \cdot t}{2L}\right) \sin \omega_n t, \quad \omega_n \approx \omega_0 \quad (Q_x \geq 3)$$
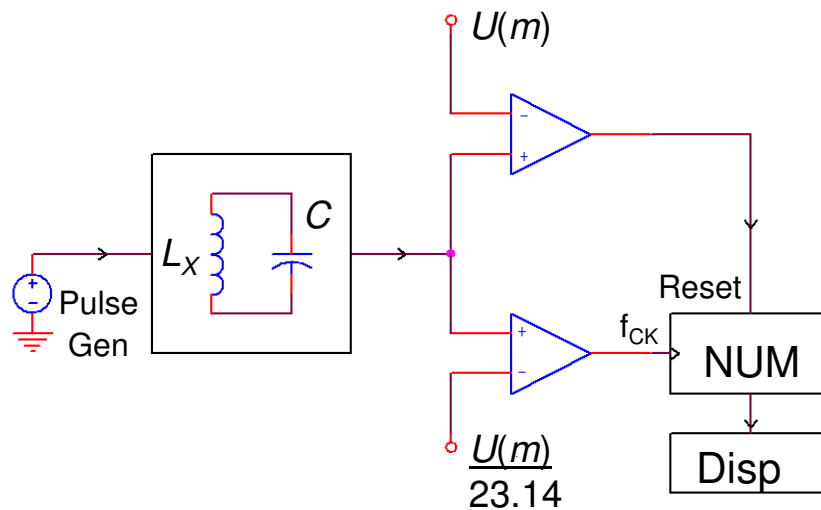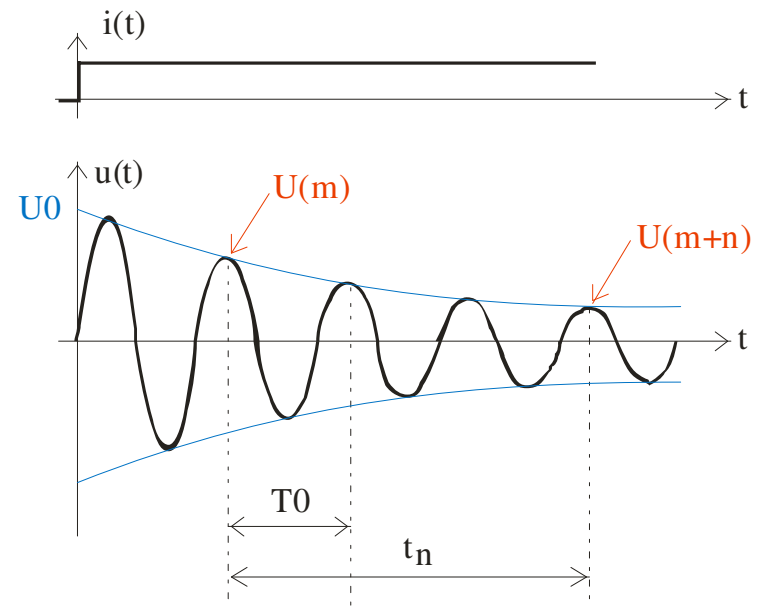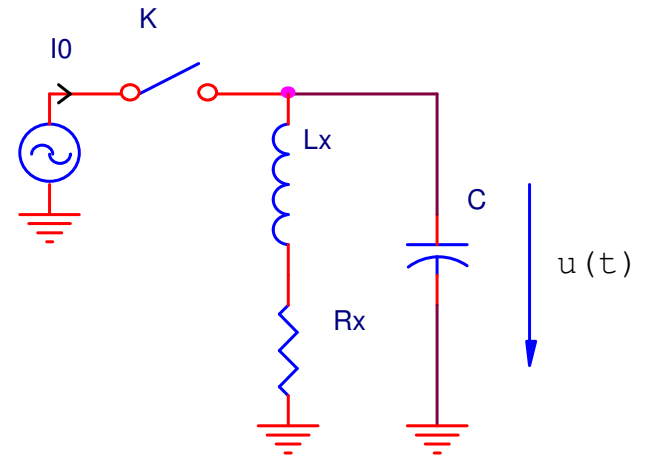
$$Q_x = n = \frac{t_n}{T_0} = \frac{Q}{\pi} \ln K \Rightarrow K = \frac{U(mT_0)}{U((m+n)T_0)} = e^\pi = 23.14$$



### ■ Auto-balancing bridge method

- DUT = device under test
- uses a signal source, a voltmeter, and an ammeter that measure vectors (magnitude and phase angle)
- The input impedance of ammeter (virtually zero) does not affect measurements
- Distributed capacitance of the test cables does not affect measurements
- Guarding technique can be used to remove stray capacitance effects

#### Advantages


- High accuracy, wide ranges of impedance
- Wide frequency ranges [20Hz-110MHz]
- Grounded device measurement

#### Disadvantages

- Higher frequency ranges not available
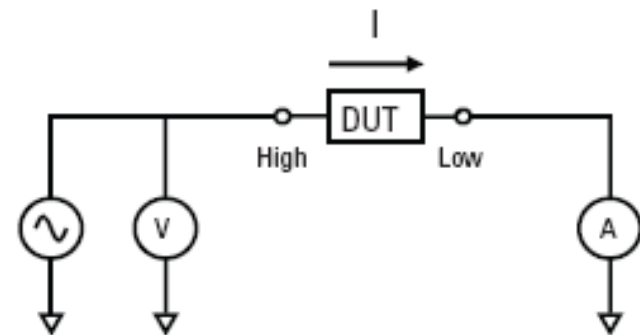
#### Applications

- Generic component measurement
- Grounded device measurement (RLC-meter)



$$Z_x = \frac{V}{I}$$



## EMI Chap 4 – Digital measurement of impedances

### ■ Auto-balancing bridge method (cont'd)

- for low frequency employs I-V converter (<100kHz) circuit and V-I converter with operational amplifier
- uses two vector voltmeters
- $R_r$ , the range resistor, determines impedance measurement range;
- $V_x$  and  $V_r$  can be measured with the same vector voltmeter (ratio detector);
- $R_r$  has known value;


$$\frac{V_x}{Z_x} = \underline{I}_x = \underline{I}_r = \frac{V_r}{R_r} \Rightarrow Z_x = \frac{V_x}{\underline{I}_x} = R_r \frac{V_r}{\underline{I}_r}$$

Auto-balancing bridge method

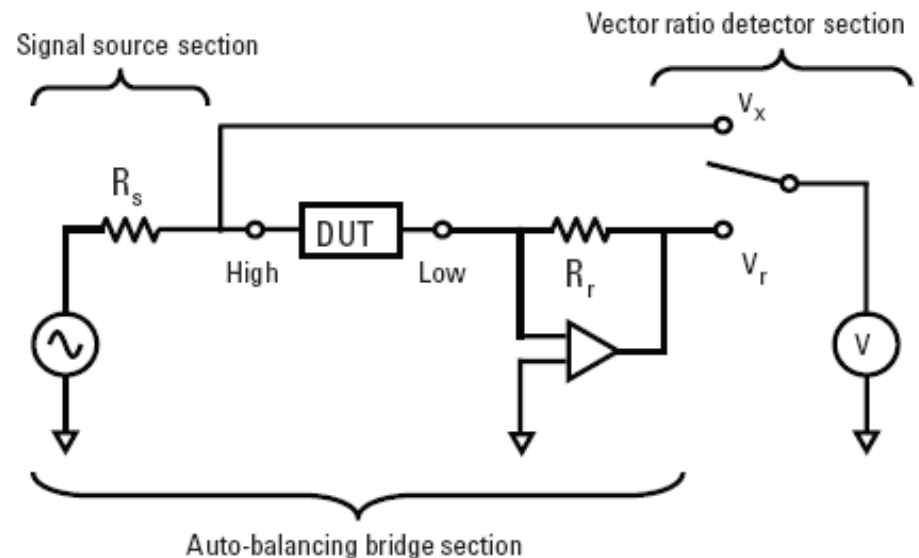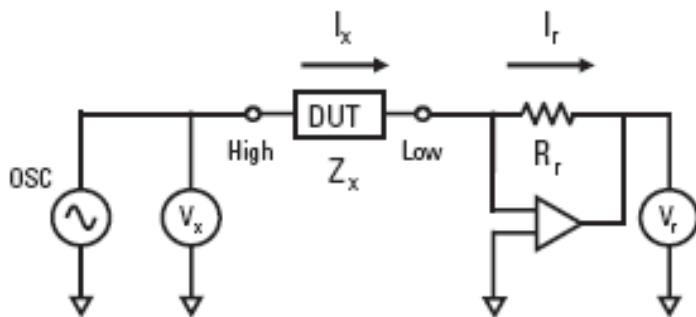

■ Auto-balancing bridge method (cont'd)




- the auto-balancing bridge section balances the range resistor current with the DUT current while maintaining a zero potential at the Low terminal;
- the null detector detects the unbalance current  $I_x - I_r$  and controls both the magnitude and phase angle of the OSC<sub>2</sub> output so that goes current to zero;
- circuit configuration cannot be used for high frequency >100kHz;
- to cover frequencies above 100 kHz the bridge employs null detector, 0°/90° phase detectors, and a vector Modulator;

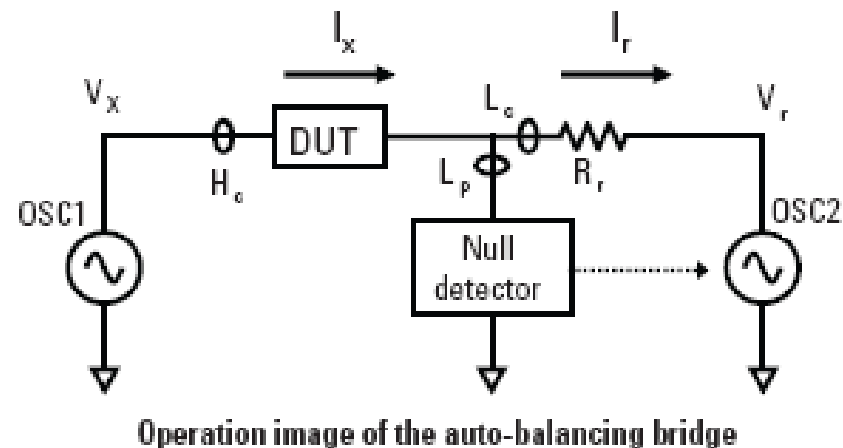

## EMI Chap 4 – Digital measurement of impedances
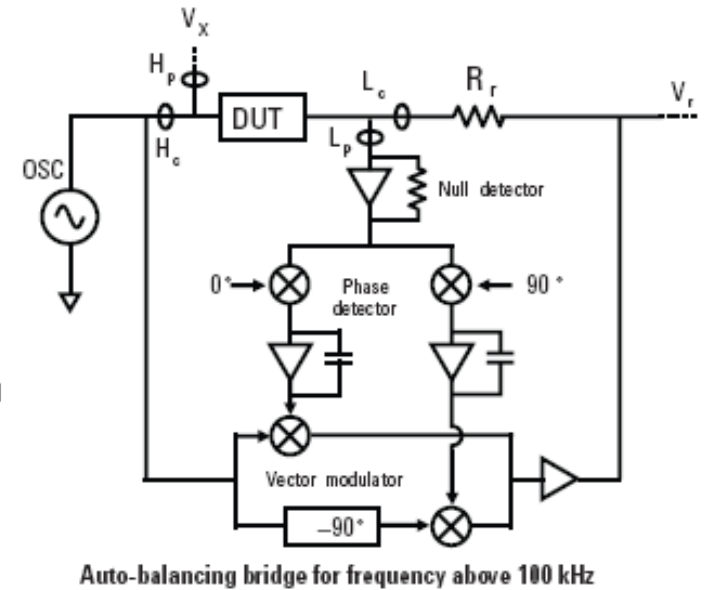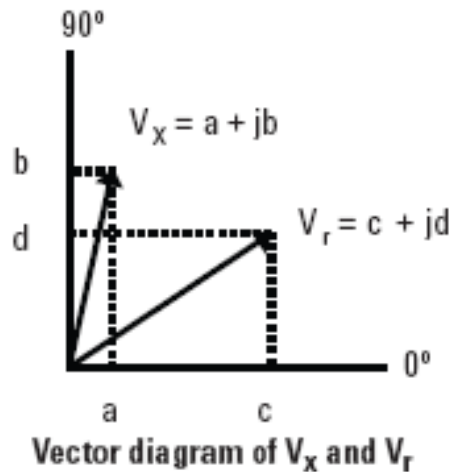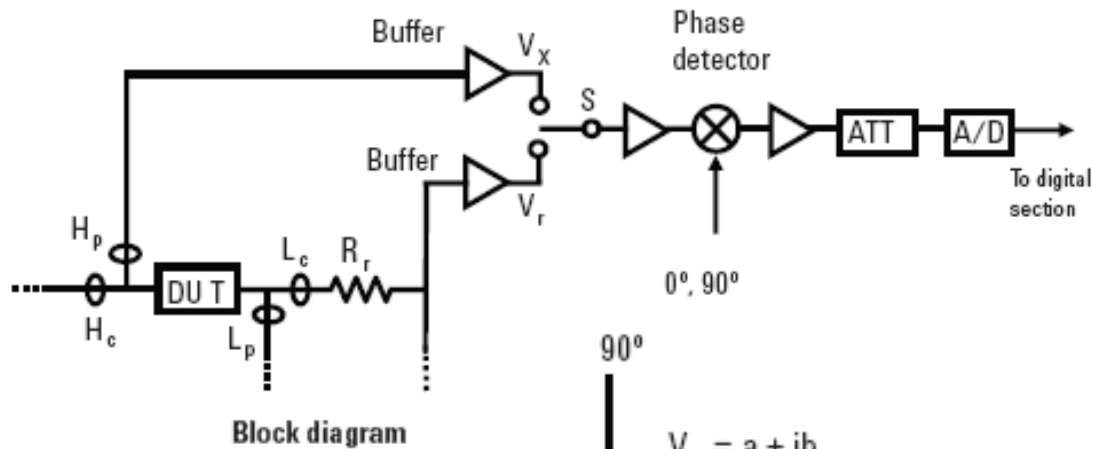
### ■ Auto-balancing bridge method (cont'd)


- the auto-balancing bridge section for high frequency measurement
- Vector ratio detector section




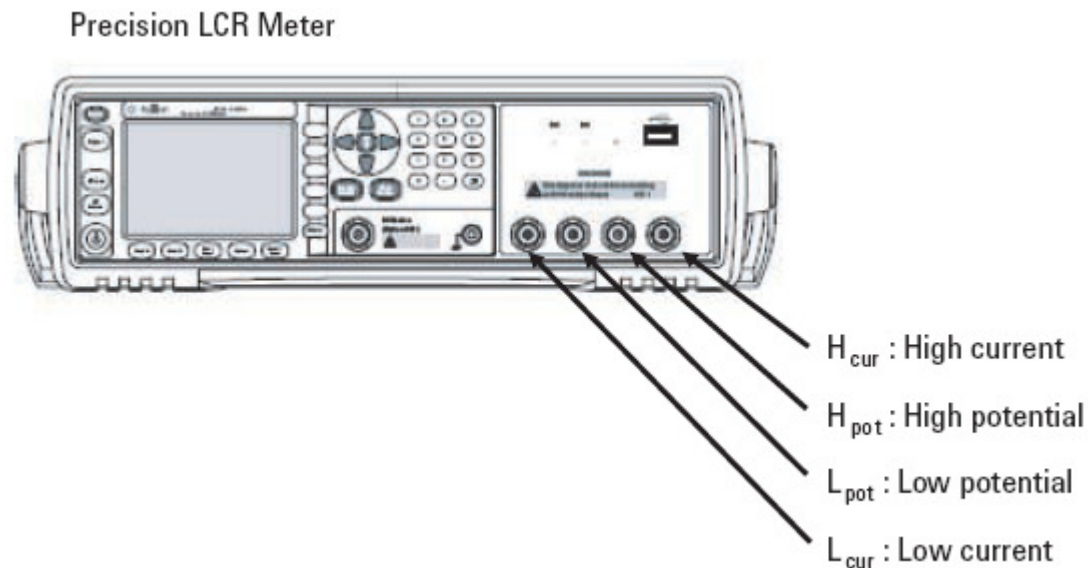
## ■ Fixturing and Cabling




- auto-balancing bridge instrument is generally equipped with four BNC connectors,  $H_{cur}$ ,  $H_{pot}$ ,  $L_{pot}$ , and  $L_{cur}$  ;



## EMI Chap 4 – Digital measurement of impedances
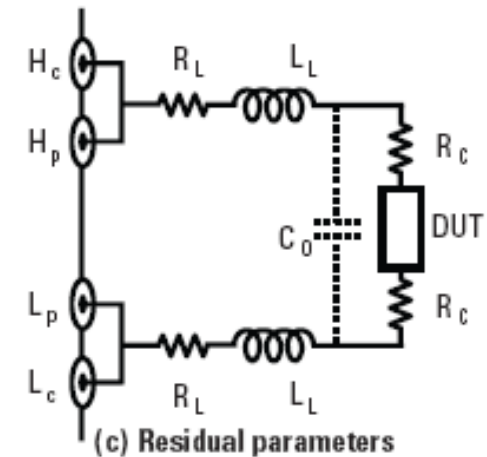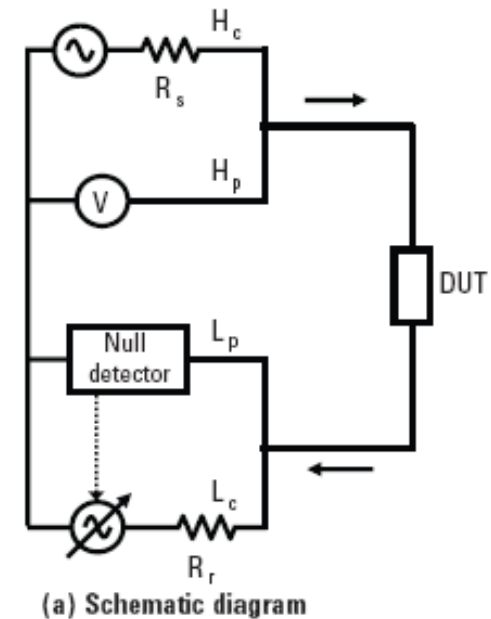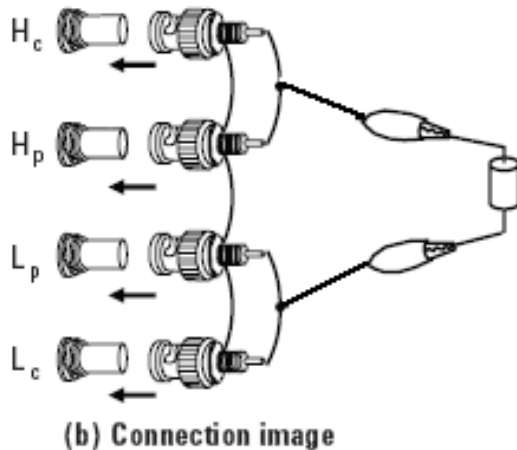
### ■ Two-terminal configuration (2T)


- is the simplest method of connecting a DUT
- contains error sources: lead inductances ( $L_L$ ), lead resistances ( $R_L$ ), stray capacitance ( $C_0$ ) between two leads and contact resistances ( $R_C$ ) between the test fixture's electrodes and the DUT;
- measurement ranges  $100\Omega - 10K\Omega$




## EMI Course 6 – Digital measurement of impedances
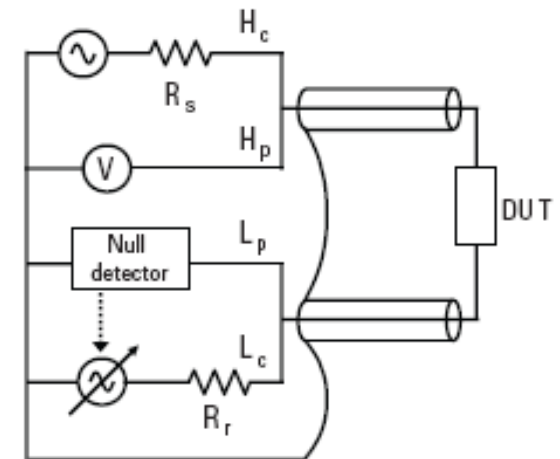
### ■ Three-terminal configuration (3T)


- employs coaxial cables to reduce the effects of stray capacitance;
- accuracy is improved for the higher impedance values;
- measurement ranges  $100\Omega - 10M\Omega$ ;



(a) Schematic diagram

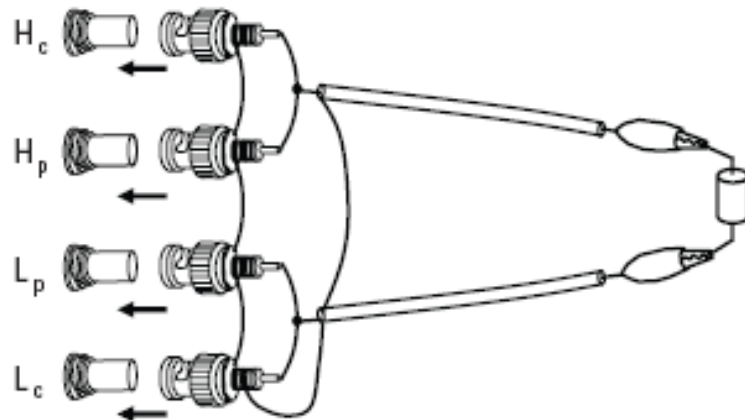


(b) Connection image

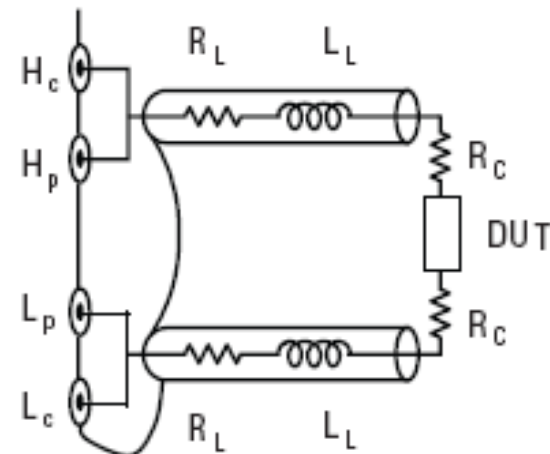


(c) Residual parameters
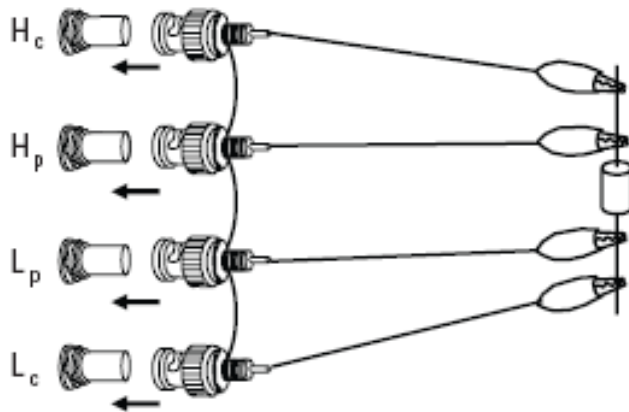
## ■ Four-terminal configuration (4T)


- the signal current path and the voltage sensing leads are independent;
- reduce the effects of lead impedances ( $\omega L_L$  and  $R_L$ ) and contact resistances ( $R_C$ );
- introduces error at low impedance measurement due mutual coupling between the leading wires
- measurement ranges 10m $\Omega$  - 10k $\Omega$ ;



(b) Connection image

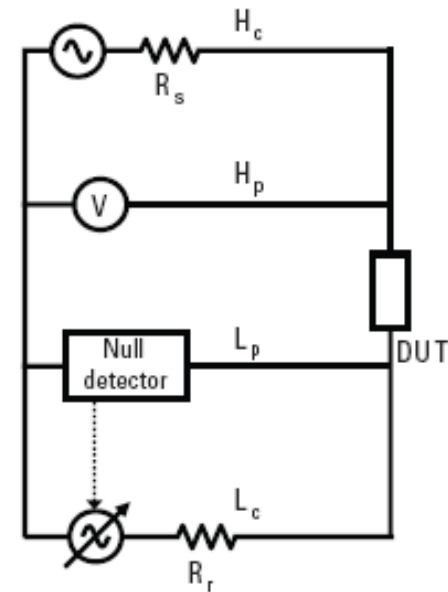


(a) Schematic diagram

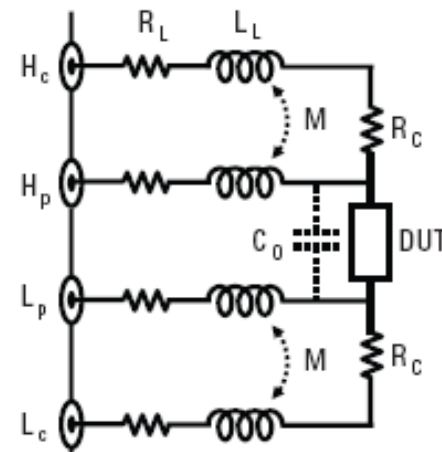


(c) Residual parameters
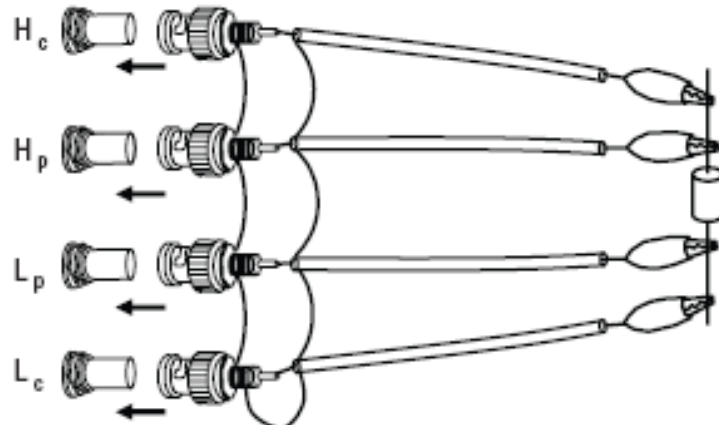
### ■ Five-terminal configuration (5T)


- employs four coaxial cables and all of the outer shielding conductors of the four cables are connected to the guard terminal
- does not resolve mutual coupling problem;
- measurement ranges  $10\text{m}\Omega$  -  $10\text{M}\Omega$ ;



(b) Connection image

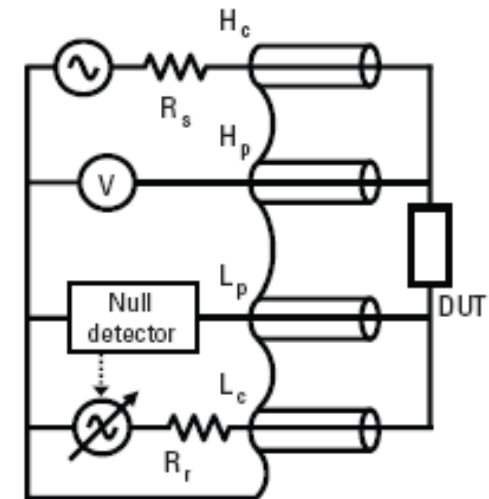

(a) Schematic diagram



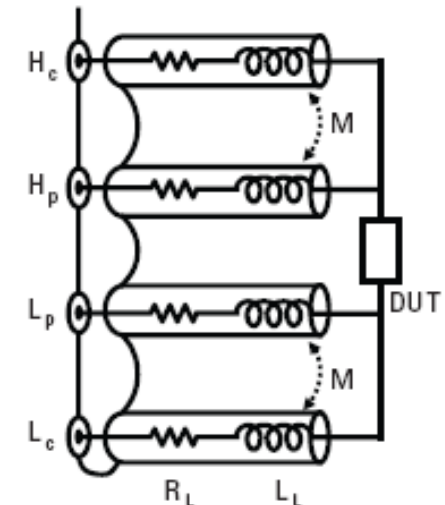


(c) Residual parameters

## EMI Chap 4 – Digital measurement of impedances
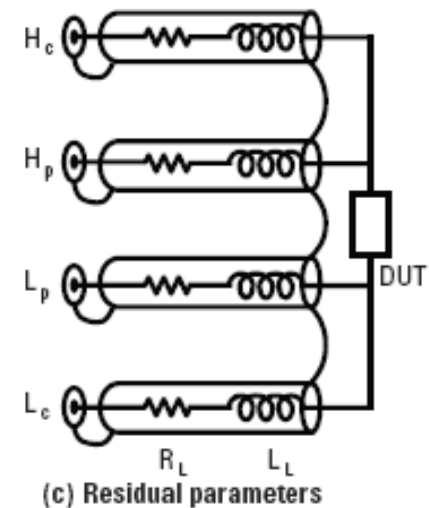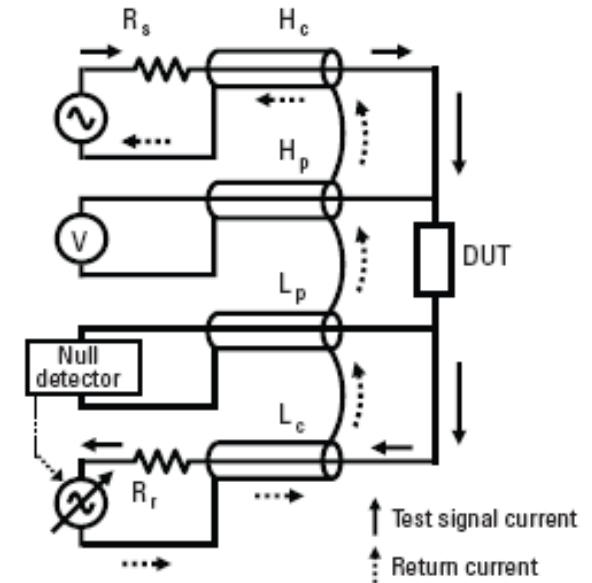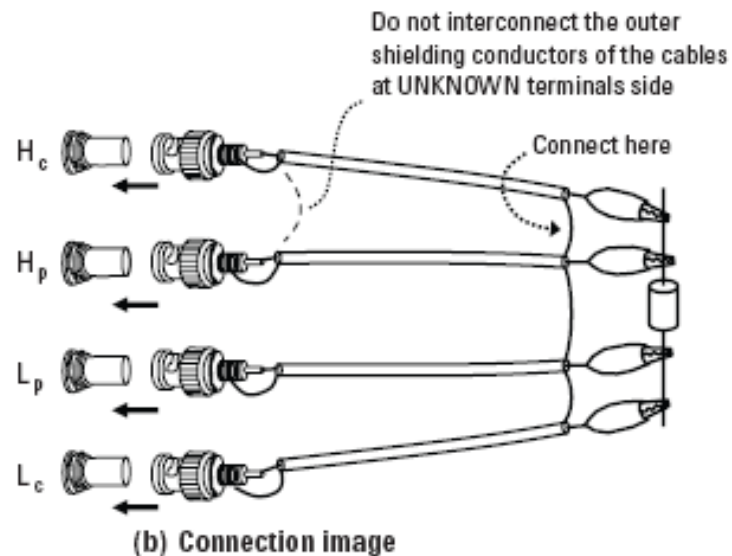
### ■ Four-terminal pair configuration (8T)

- employs four coaxial cables to reduce the effects of stray capacitance;
- connects the outer shielding conductors to each other at the ends of the coaxial cables,
- isolate outer conductors at  $H_c$ ,  $H_p$ ,  $L_p$ , and  $L_c$  terminals
- solves the mutual coupling between the leads
- measurement ranges  $1\text{m}\Omega - 10\text{M}\Omega$ ;



■ **Bibliography**

- Agilent Impedance Measurement Handbook 4'th Ed, (<http://education.tm.agilent.com>) ;
- S. Ciochina, *Masurari elettrice si electronice*, 1999;